

Name: _____

Date: _____ 20

Examination: _____ Branch/Semester: _____


Subject: _____

Junior Supervisor's full
Signature with Date

Question No.	1	2	3	4	5	6	7	8	9	10	11	12	Total
Marks Obtained	10	10	10	10	10	10	10	10	10	10	10	10	10

AC Circuits

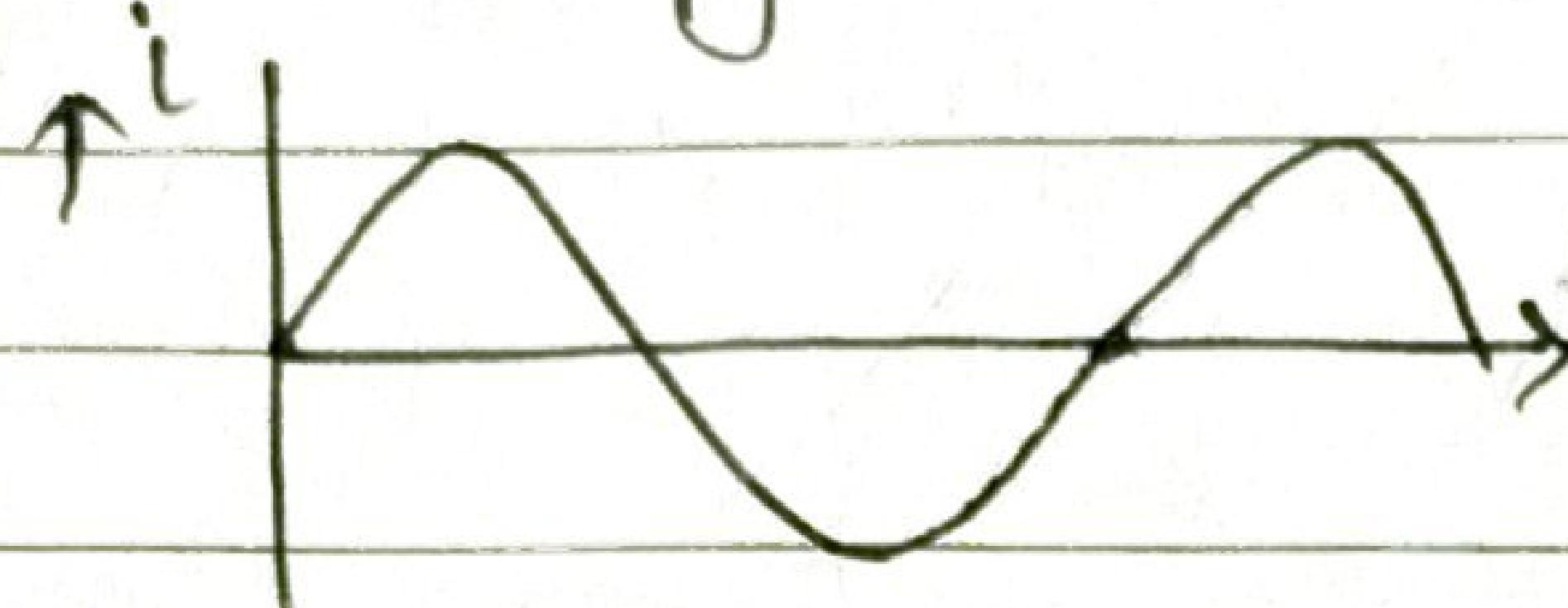When current flowing in the circuit varies in magnitude as well as direction periodically is called alternating current.




A volg. that changes its polarity at regular intervals of time is called as alternating volg.

Advantages of AC

- Voltages in this system can be raised or lowered with the help of a transformer.
- High voltage ac transmission is possible and economical through the use of transformers.
- AC motors are simple, cheap and require less attention from maintenance point of view.
- AC supply can be easily converted into a dc supply.

Sinusoidal Alternating Voltage and Current

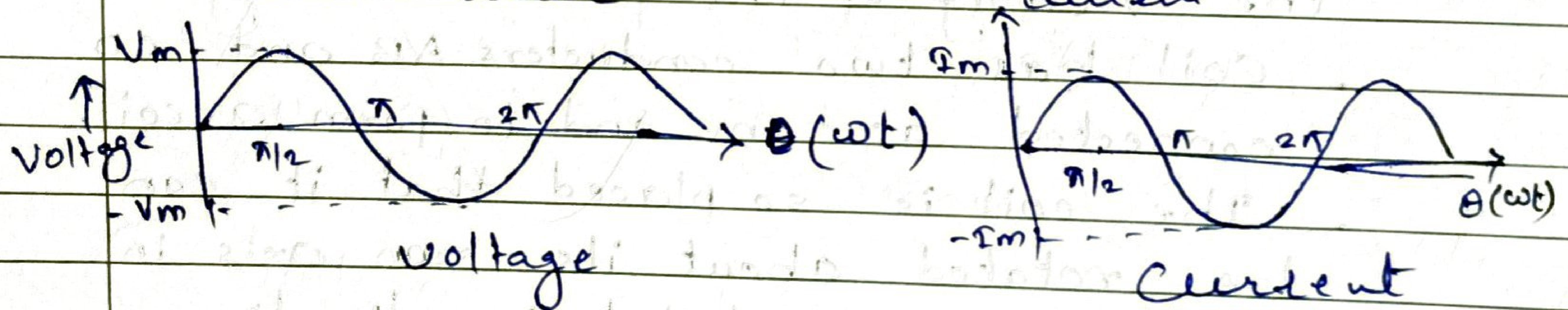- A sinusoidal alternating quantity is one whose instantaneous value varies according to the sine function of time. i.e. it produces a sine wave.



Mathematical eq's

$$v = V_m \sin \omega t$$

where v = Instantaneous value of alternating voltage

V_m = Max. value of alternating voltage

ω = Angular velocity of coil


V_m and ω are constant.

Similarly alternating current varying sinusoidally can be expressed as

$$i = I_m \sin \omega t$$

Ac Generator :-

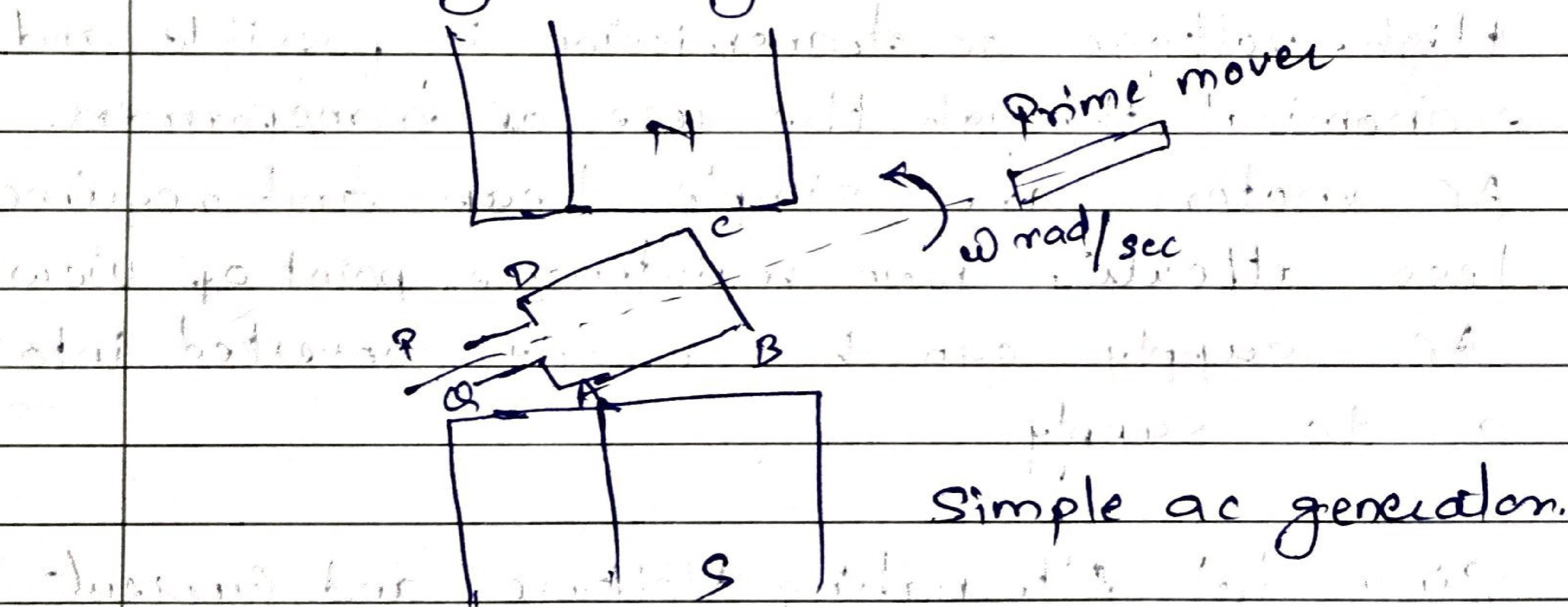Machine used to generate a sinusoidal alternating voltage.



- It consists of a permanent magnet of two poles.
- A single rectangular coil is placed in the vicinity of the permanent magnet.
- Coil has two conductors AB and CD connected at one end to form a coil.
- The coil is so placed that it can be rotated about its own axis in clockwise or anticlockwise direction.

P & Q are the ends of the coil.
 When the coil is rotated in anticlockwise direction with constant angular velocity (by means of prime mover) in a uniform magnetic field, its conductors AB and CD cut the magnetic lines of flux and according to Faraday's laws of electromagnetic induction, emf gets induced in them.

$$\text{emf induced in one conductor} = BLV \sin\theta$$

Assuming two conductors identical

Total emf induced in a coil

$$v = 2BLV \sin\theta \quad \dots \quad \begin{matrix} \omega = \text{angular} \\ \text{velocity rad/sec} \end{matrix}$$

When $\theta = 90^\circ$, induced emf is

max. $\therefore V_m$

$$\therefore V_m = \text{max. value of induced emf}$$

$$\therefore V_m = 2BLV \sin 90^\circ$$

$$V_m = 2BLV$$

\therefore Eqn (1) becomes

$$v = V_m \sin\theta \quad \dots \quad \begin{matrix} B = \text{Flux density of} \\ \text{mag. field.} \end{matrix}$$

This is the instantaneous value of emf induced in a coil.

θ continuously varies from 0° to 360° .

\therefore the magnitude of induced emf in coil continuously varies.

$$\theta = 0^\circ \quad v = 0 \text{ volt}$$


$$\theta = 45^\circ \quad v = 0.707 V_m \text{ volts}$$

$$\theta = 90^\circ \quad v = V_m \text{ Volts}$$

$$\theta = 180^\circ \quad v = 0 \text{ Volts}$$

$$\theta = 270^\circ \quad v = -V_m \text{ Volts}$$
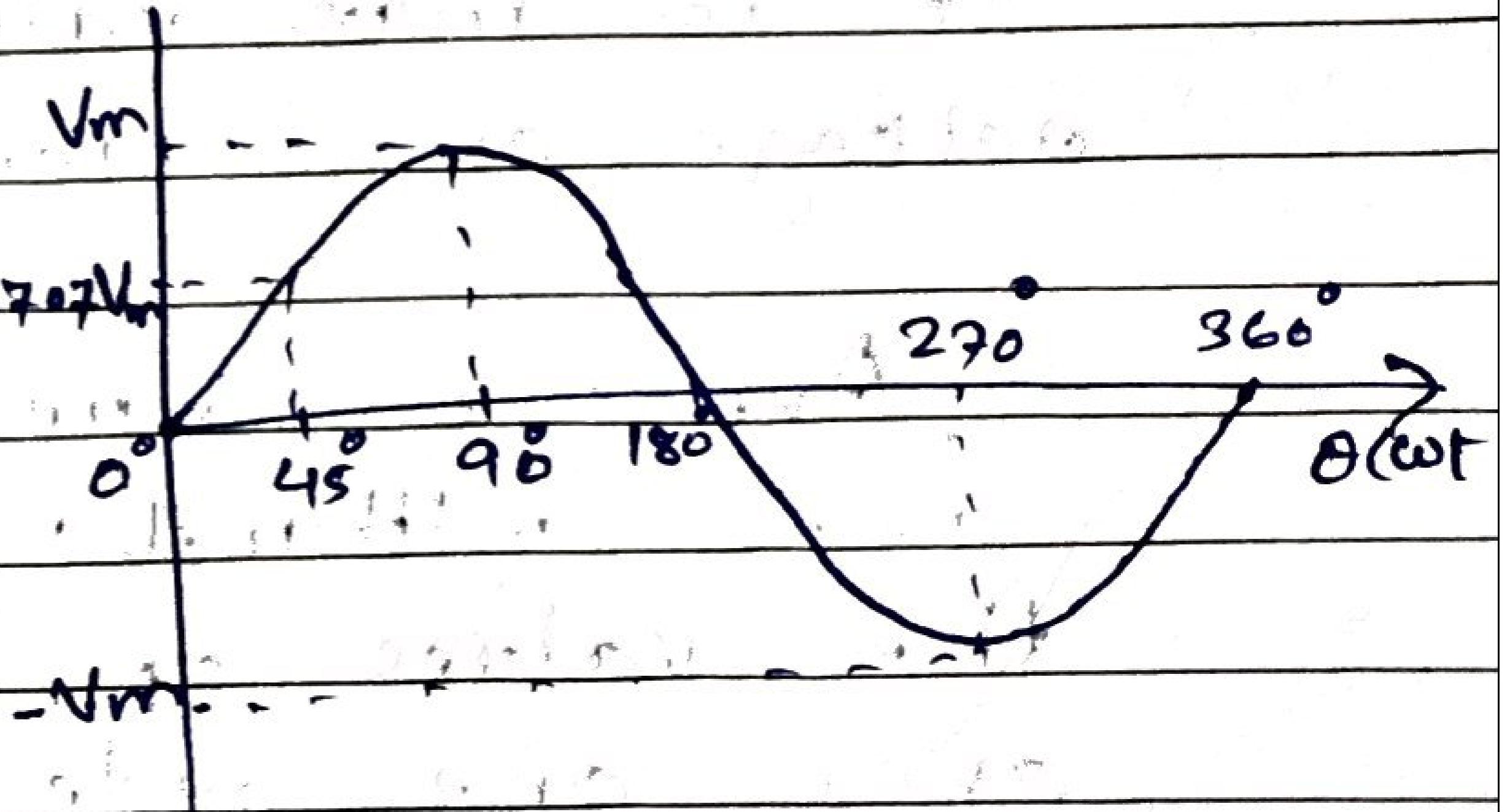
$$\theta = 360^\circ \quad v = 0 \text{ Volts}$$



Standard forms of alternating quantity

ω = angular velocity rad/sec

Angle turned by the coil

$$\theta = \omega t \text{ rad}$$

Time taken to complete one cycle is the time period T of the alternating volg.

$$\text{Angular velocity } \omega = \frac{\text{Angle turned}}{\text{Time taken}} = \frac{2\pi}{T}$$

$$\text{or } \omega = 2\pi f \quad (f = \frac{1}{T})$$

Standard forms of sinusoidal alternating volg are given by

$$v = V_m \sin \theta$$

$$v = V_m \sin \omega t$$

$$v = V_m \sin 2\pi f t$$

$$v = V_m \sin \frac{2\pi}{T} t$$

Values of alternating voltage and current :-

Magnitude of alternating voltage or current is expressed by 3 ways:

1. Peak value

2. Average value

3. r.m.s value or effective value

1. Peak value:-

It is max. value attained by alternating voltage or current. It is V_m or I_m .

2. Average value:-

The arithmetical average of all the values of alternating quantity over one cycle is called its average value.

$$\text{Average value} = \frac{\text{Area under the wave}}{\text{Base}}$$

For symmetrical waveforms (+ve half = -ve half)

$$\text{Average value} = \frac{\text{Area of half cycle}}{\text{Base length of half cycle}}$$

For unsymmetrical waveforms (+ve half ≠ -ve half)

$$\text{Average value} = \frac{\text{Area of full cycle}}{\text{Base length of full cycle}}$$


3. rms value or effective value:-

Rms value of current is equal to that direct current which when flowing thr' a given resistance for a given time produces the same amount of heat as produced by ac when flowing thr' the same resistance for the same time.

For symmetrical waveform

$$\text{Rms value} = \sqrt{(\text{Average value})^2}$$
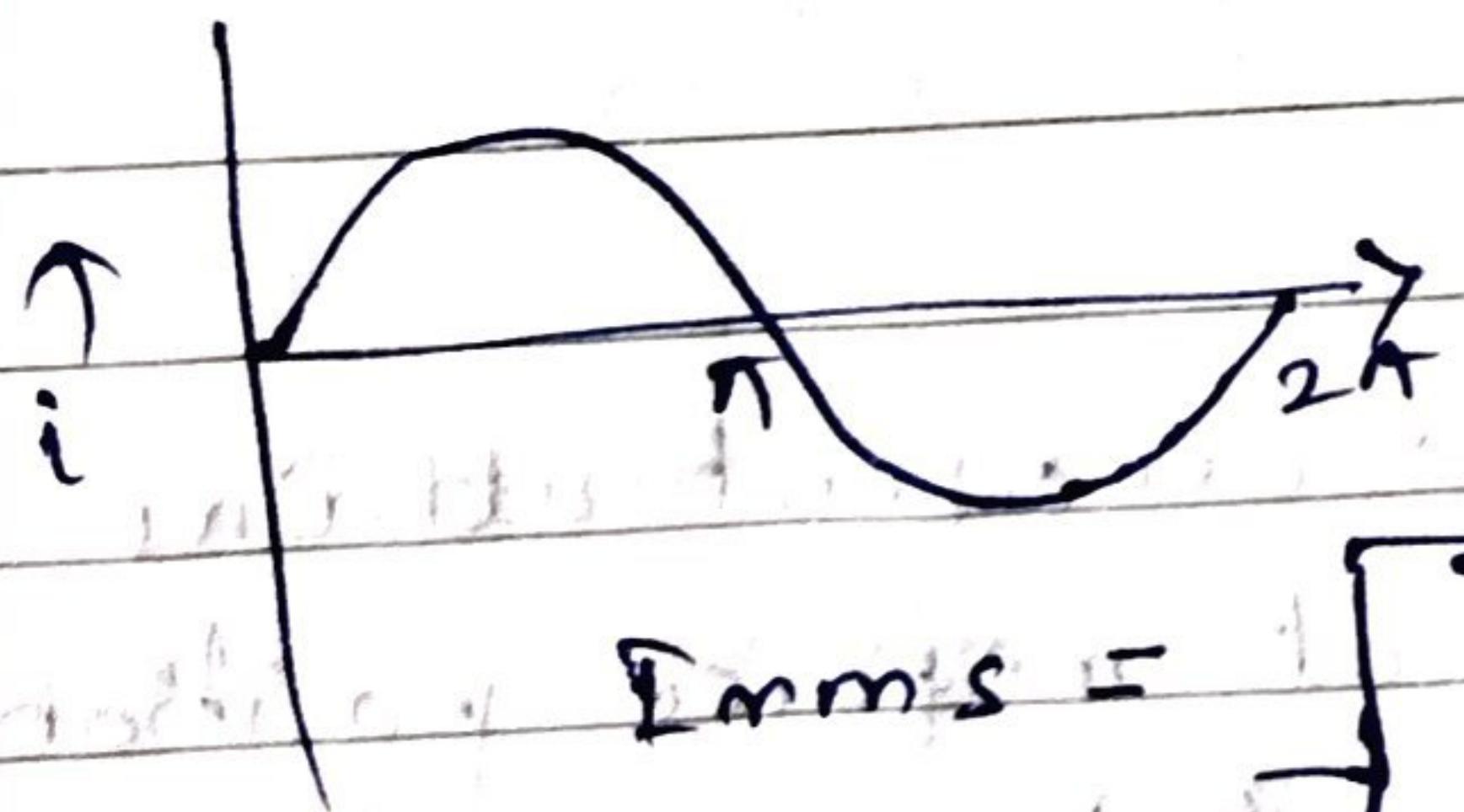
$$= \sqrt{\frac{\text{Area of half/full cycle of squared wave}}{\text{Base length of half/full cycle}}}$$



$$I_{rms} = \sqrt{\frac{\int_0^{\pi} i^2 d\theta}{\pi}}$$

$$I_{rms} = \frac{1}{\pi} \int_0^{\pi} I_m^2 \sin^2 \theta d\theta$$

$$I_{rms} = I_m = \frac{0.707 I_m}{\sqrt{2}}$$

Similarly

$$V_{rms} = \frac{V_m}{\sqrt{2}} = 0.707 V_m$$

Form Factor and Peak factor

Relationship among peak value, average value and the rms value of alternating quantity.

1) Form factor :- It gives peakiness of the waveform.

$$\text{Form factor} = \frac{\text{rms value}}{\text{Average value}}$$

$$\text{e.g., for sinusoidal volg. or current}$$

$$\text{Form factor} = 0.707 \times \text{Max value} = 1.11$$


$$= 0.637 \times \text{Max value}$$

2) Peak factor = $\frac{\text{Max. value}}{\text{rms value}}$

e.g. for sinusoidal volg. or current

$$\text{Peak Factor} = \frac{\text{Max. value}}{0.707 \times \text{Max Value}} = 1.414$$

Phase Angle and Phasor :-

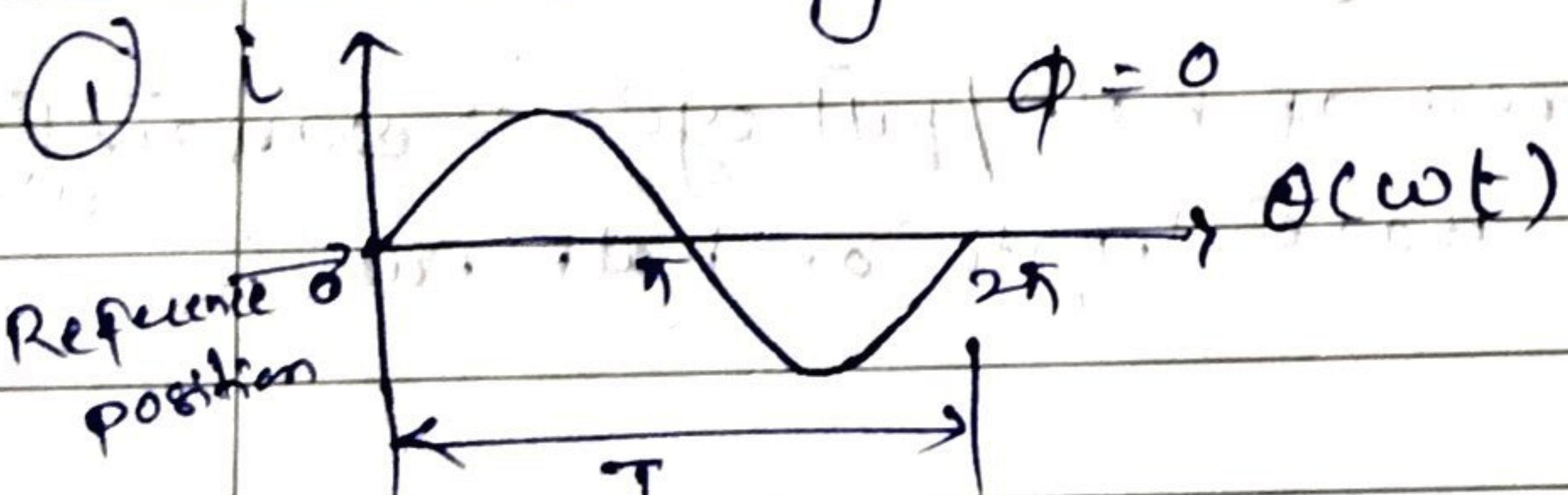

$$i = I_m \sin(\omega t + \phi)$$

In above case $\phi = 0$ ∴ current attains its zero value exactly at reference position.

∴ phase angle of current is zero.


Alternating current/volg. can be represented by Phasor.



- Length of phasor represents magnitude i.e. rms value.

- Inclination w.r.t. reference axis is equal to the phase angle of that quantity.


(2)

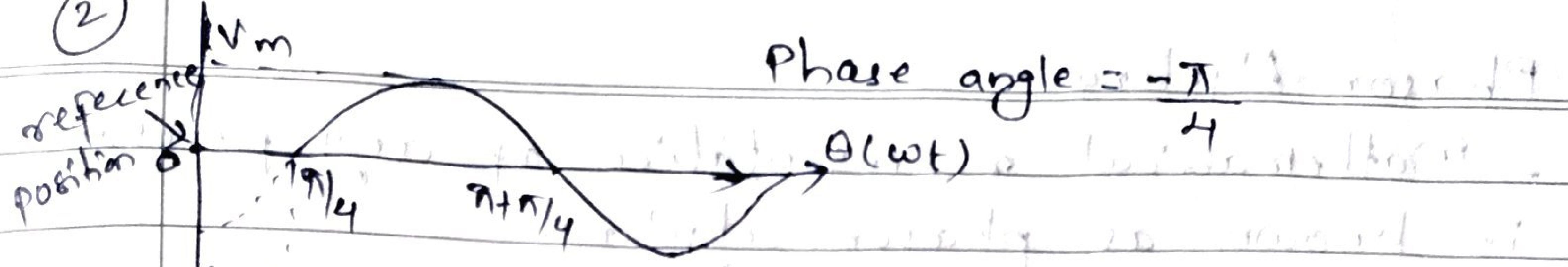


Volg. attains its zero value (first time) after a reference position by angle $\pi/4$ rad or 45° means it lags behind reference. so phase angle $\phi = -\frac{\pi}{4}$ rad or -45°

$$v = V_m \sin(\omega t - \frac{\pi}{4}) \text{ or } v = V_m \sin(\omega t - 45^\circ)$$

Voltage phasor is

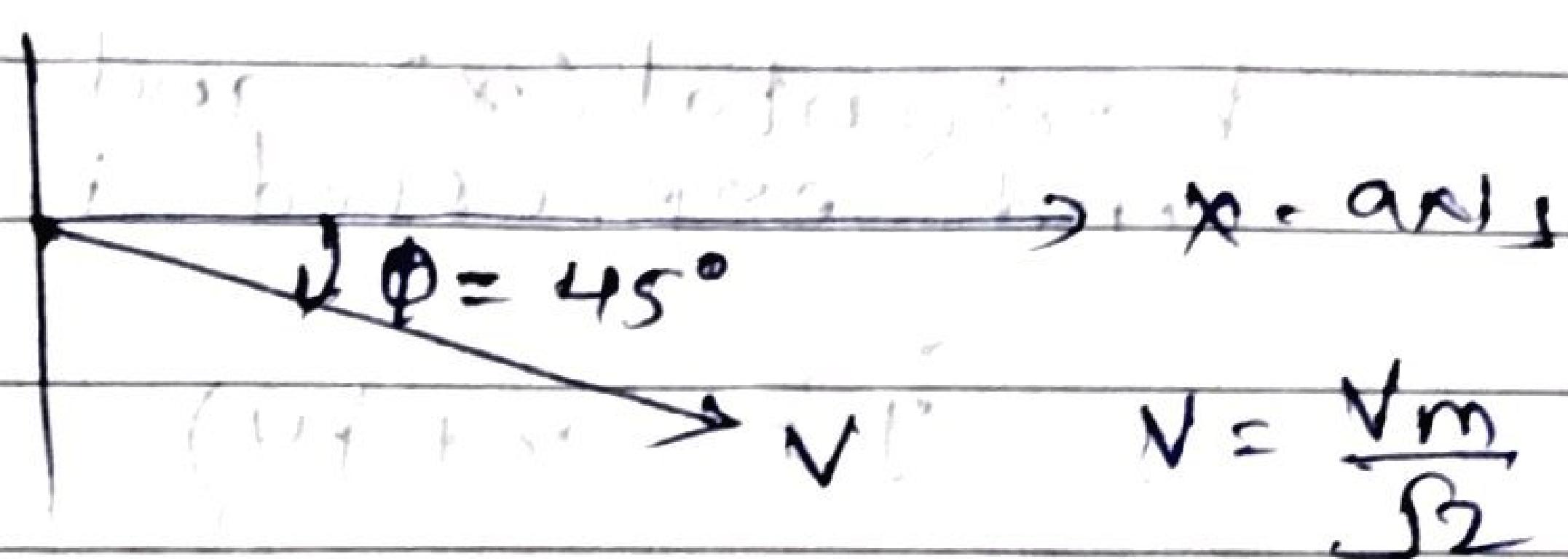


(3)

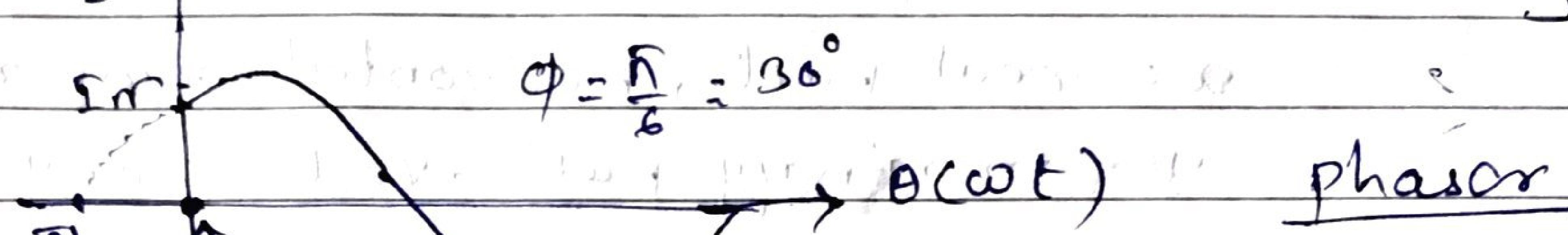



reference position
 ϕ

$$i = I_m \sin(\omega t + \frac{\pi}{6}) \quad \text{or} \quad i = I_m \sin(\omega t + 30^\circ)$$


phasor

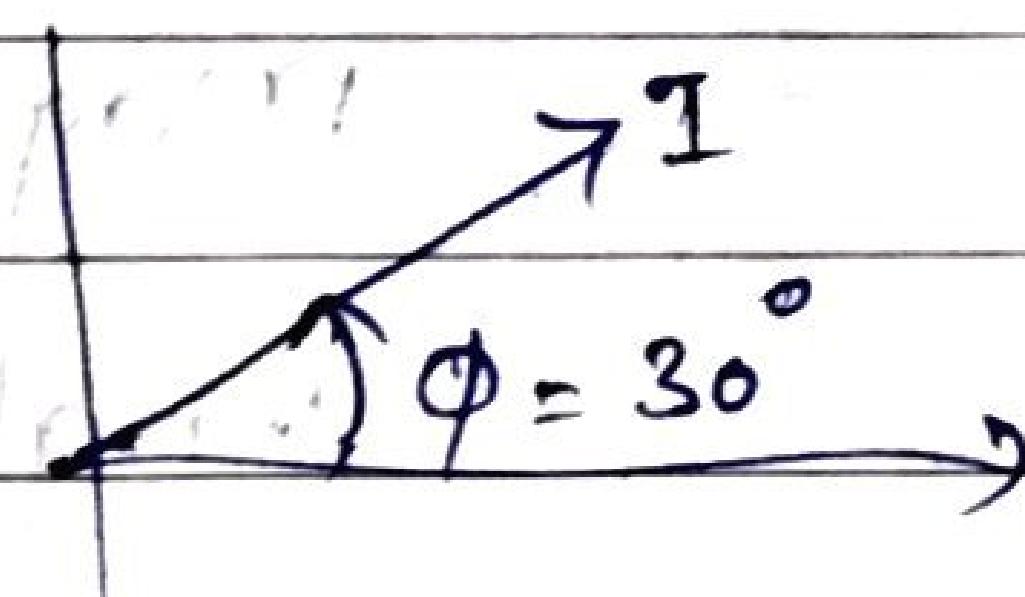

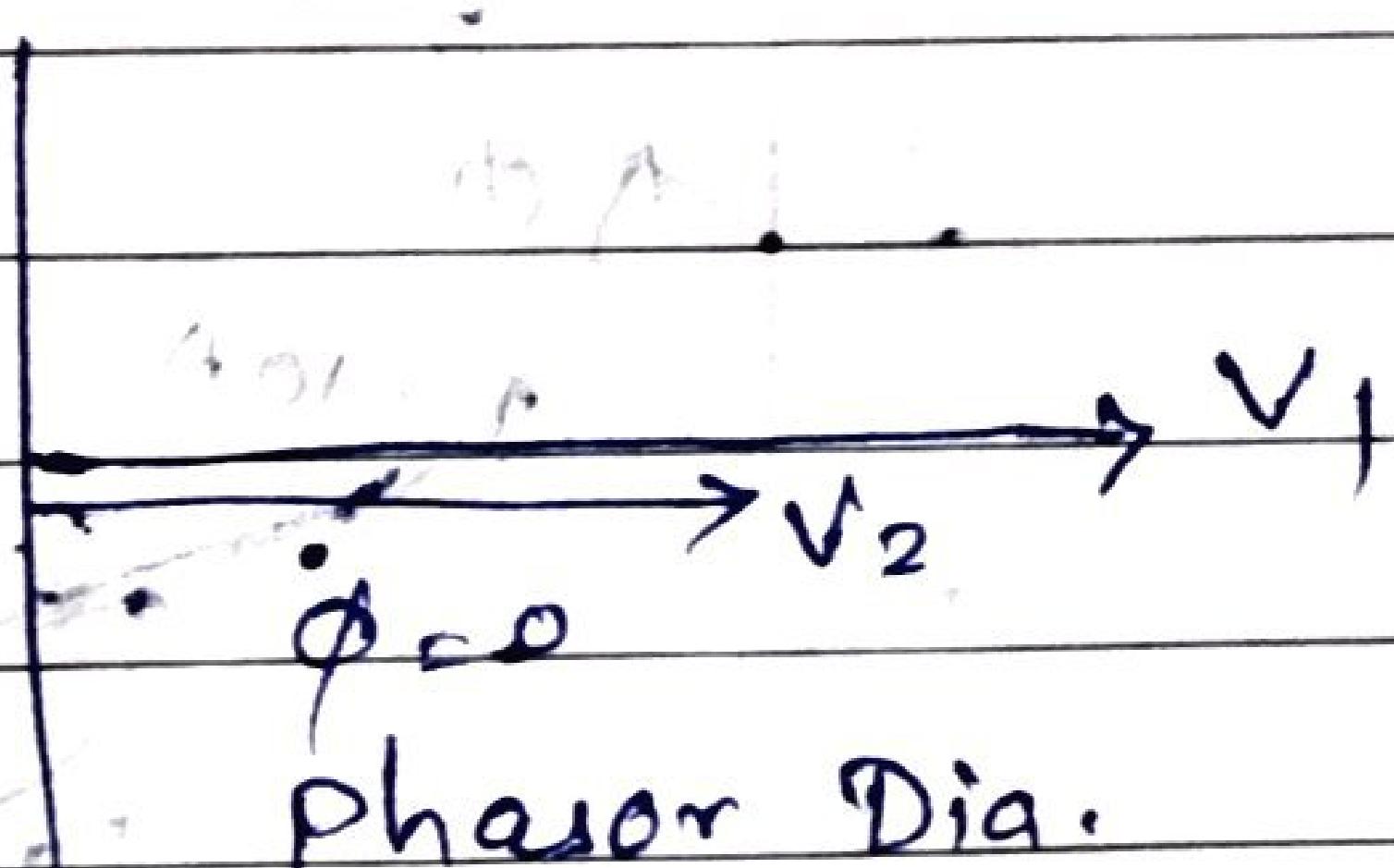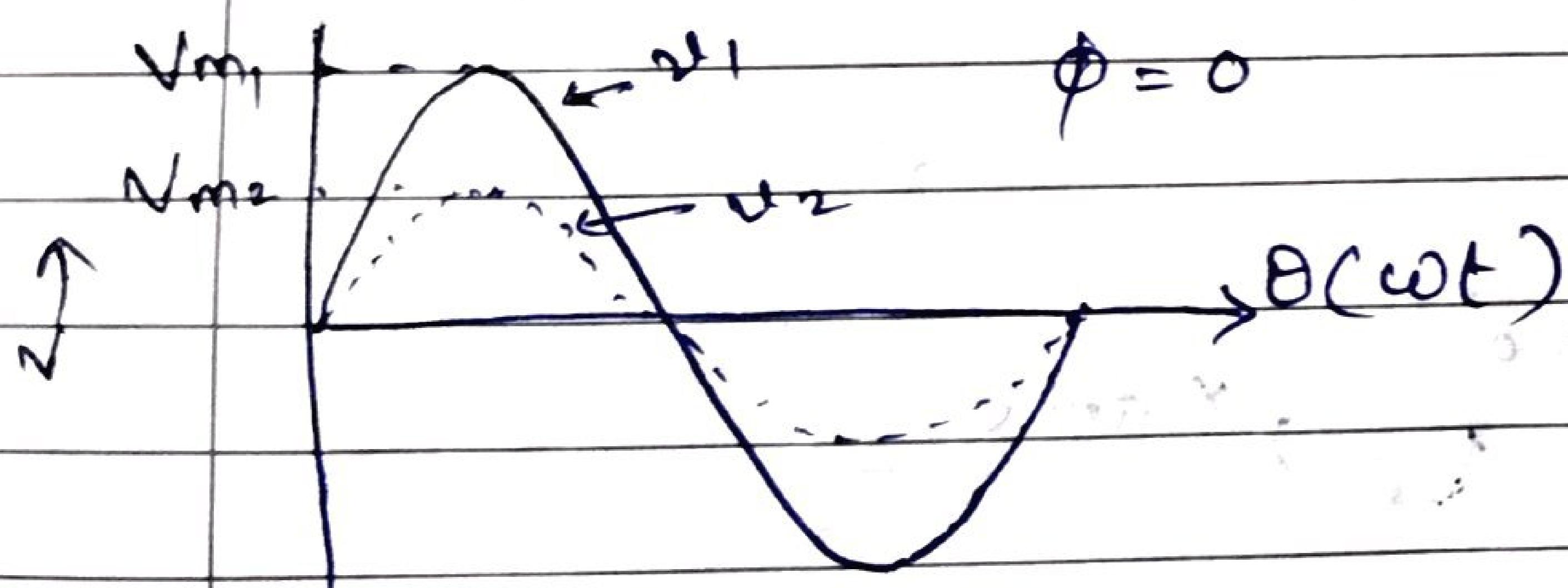In phase, Out of phase and phase difference



Voltages in phase.

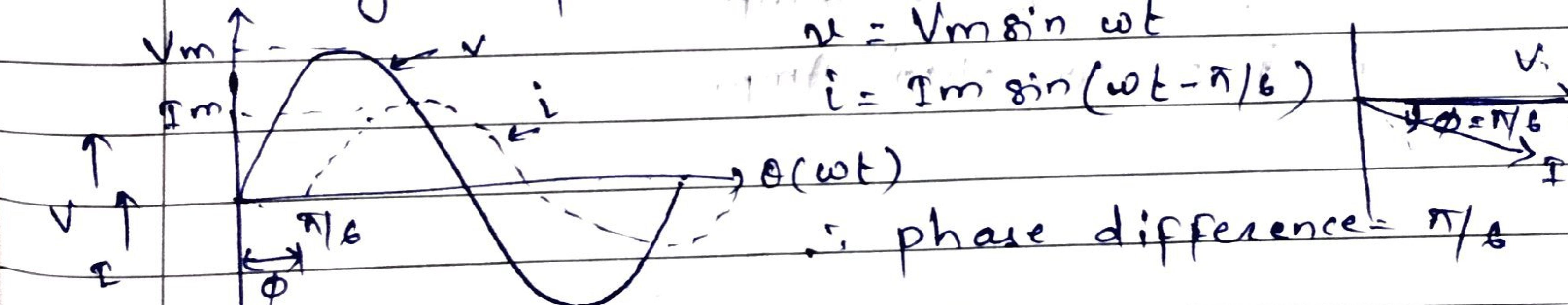

$$v = V_m \sin \omega t$$

$$i = I_m \sin(\omega t - \pi/6)$$

\therefore phase difference = $\pi/6$

Voltage is leading current or current is lagging volg. by $\phi = 30^\circ$

Phasor Algebra


- Mathematical representation of any phasor is known as phasor algebra.

Two ways:

1) Rectangular form and 2) Polar form.

1) Rectangular form

It is a complex form.

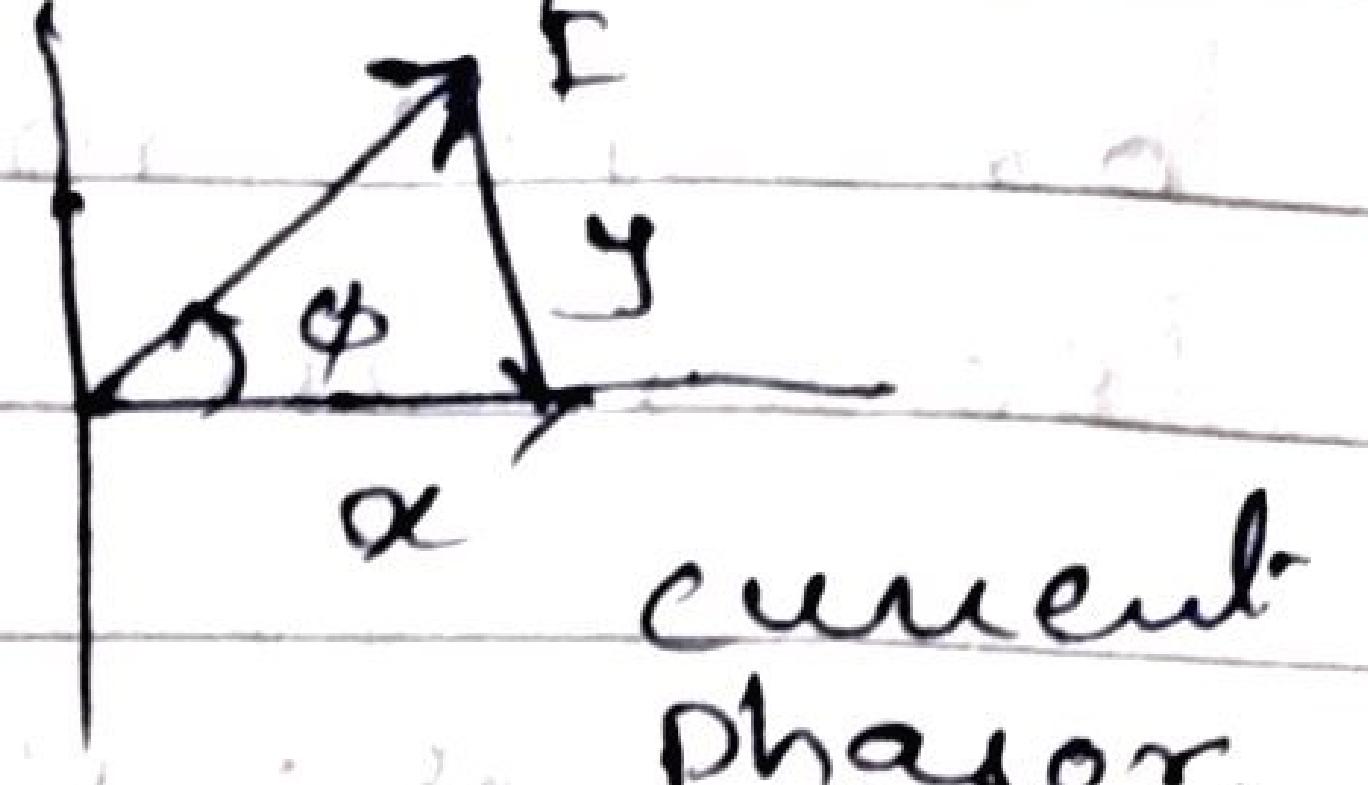

In this form, the phasor

is resolved into two components:

horizontal (x) and vertical (y) components.
and expressed in complex form.

$$\bar{I} = (x + jy)$$

x = real part, horizontal component, x -component

y = imaginary part, vertical or y -component


$$\text{Magnitude of phasor} = I = \sqrt{x^2 + y^2}$$

$$\text{Angle w.r.t. } x\text{-axis} = \phi = \tan^{-1} \frac{y}{x}$$

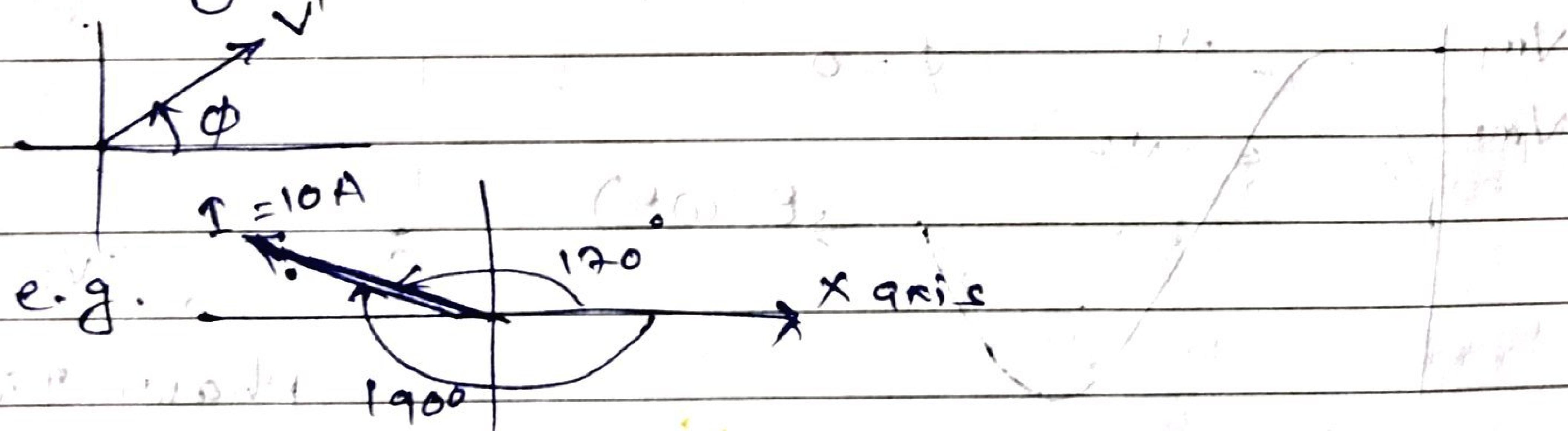2) Polar Form.

Current ^{phasor} is represented as I / ϕ

Voltage phasor is written as $V L + \phi$



$$\bar{I} = 10 \angle 170^\circ \text{ Amp}$$

$$\text{or } \bar{I} = 10 L - 190^\circ \text{ Amp.}$$

Name: _____


Date: _____ 20

Examination: _____ Branch/Semester _____

Junior Supervisor's full
Signature with Date

Subject: _____

Question No.	1	2	3	4	5	6	7	8	9	10	11	12	Total
Marks Obtained													

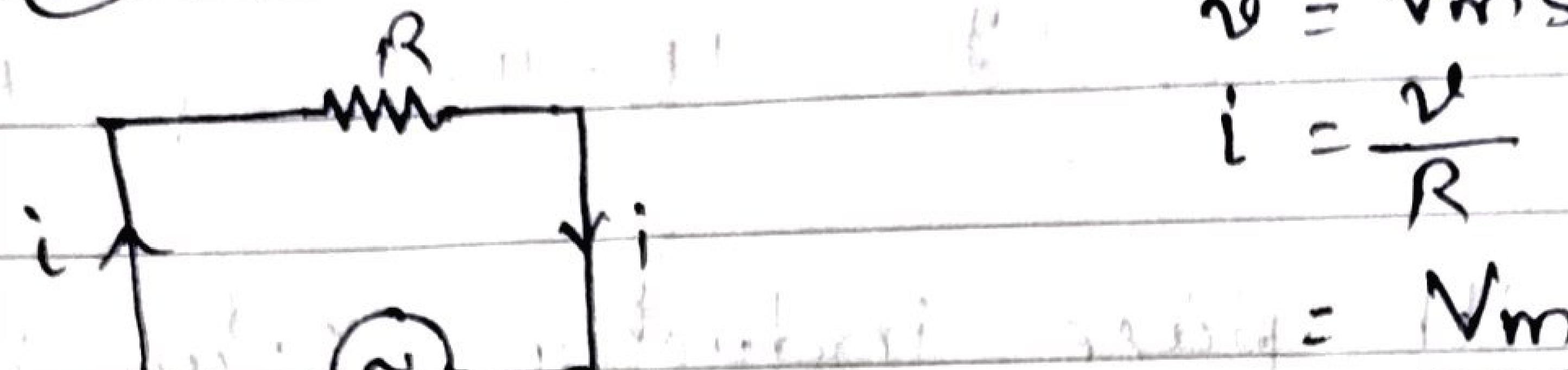Fundamental AC circuits:-① AC circuit with Resistance

$$v = V_m \sin \omega t \quad \text{--- (1)}$$


$$i = \frac{v}{R}$$

$$i = \frac{V_m \sin \omega t}{R} \quad \text{--- (2)}$$

At $\omega t = 90^\circ$, i will be max. when $\sin \omega t = 1$

$$\text{Current amplitude } I_m = \frac{V_m}{R} \quad \text{--- (3)}$$

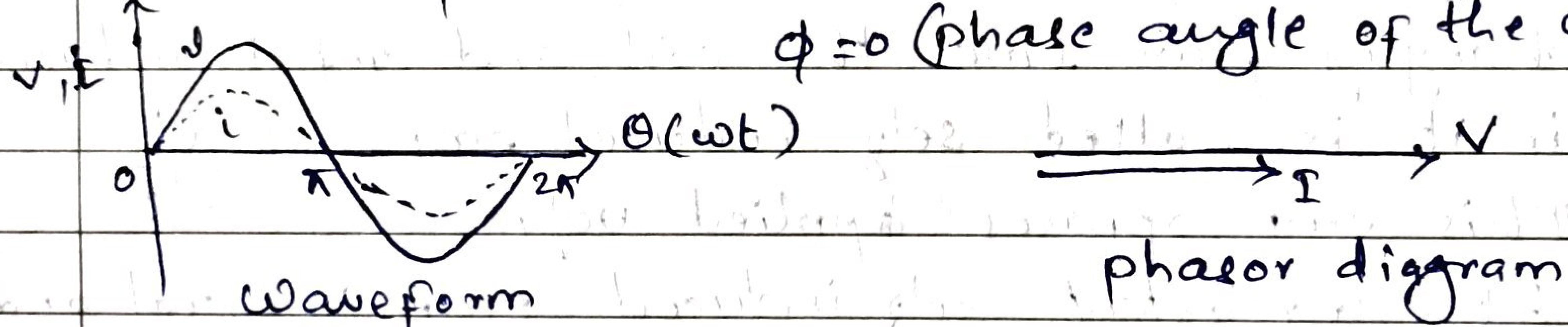From eq's (1) & (3) it can be found that the applied voltage and the circuit current are in phase with each other. i.e. $\phi = 0$
 $\phi = 0$ (phase angle of the ckt)



Impedance (Z): - Opposition offered by a circuit element to the current flow.

$$\underline{V} = Z \underline{I}$$

for resistive ckt $Z = R$

Power (P): - $P = V_i \cos \phi$

$$\text{instantaneous power} = (V_m \sin \omega t) \cdot (I_m \sin \omega t)$$

$$= V_m I_m \sin^2 \omega t$$

$$= V_m I_m \left(\frac{1 + \cos 2\omega t}{2} \right)$$

$$= \frac{V_m I_m}{2} + \frac{V_m I_m \cos 2\omega t}{2}$$

Power is a scalar quantity, average power over a complete cycle is to be considered.


$$\therefore \text{Power consumed } P = \frac{1}{2\pi} \int_0^{2\pi} P_{\text{avg}} dt$$

$$= \frac{1}{2\pi} \int_0^{2\pi} \left[\frac{V_m I_m}{2} - \frac{V_m I_m}{2} \cos 2\omega t \right] dt$$

$$= \frac{V_m \times I_m}{2} \sqrt{2}$$

$\therefore P = VI$ V - rms value of applied voltage
 I - rms value of current

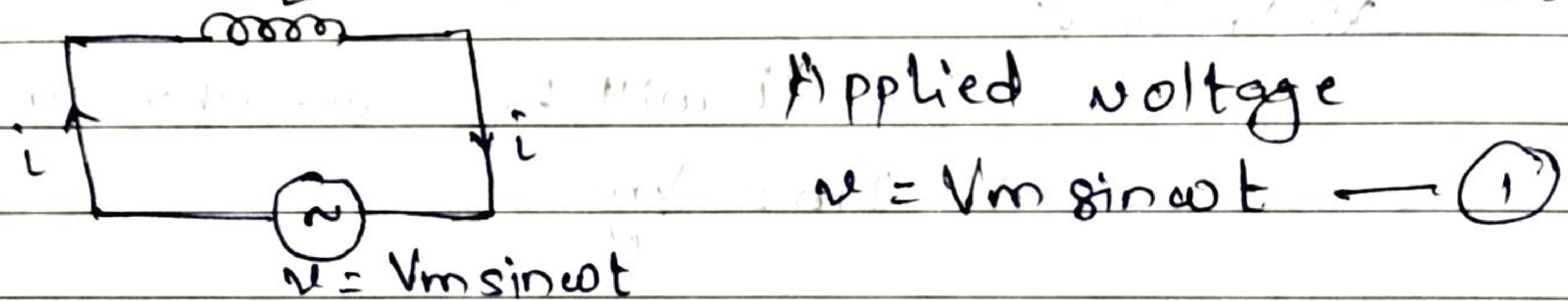Ac circuit with pure inductance (Pure inductor)



As a result of this voltage alternating current i flows through the inductance L .

Alternating current sets up alternating magnetic field around the inductance. This changing flux links the coil and emf is induced in it. It is called self-induced emf $= L \frac{di}{dt}$. This emf opposes applied volg.

At any instant self induced emf is equal and opposite to the applied volg.

$$\therefore +v = L \frac{di}{dt}$$

$$L di = +v dt$$

$$L di = V_m \sin \omega t dt$$

$$di = \frac{V_m}{L} \sin \omega t dt$$

Integrating both sides

$$i = \frac{V_m}{L} \int \sin \omega t dt$$

Power factor has magnitude and nature. Magnitude equals to $\cos\phi$. Nature is same as nature of current.

$$i = \frac{V_m}{\omega L} (-\cos\omega t)$$

$$\therefore i = \frac{V_m}{\omega L} \sin(\omega t - \frac{\pi}{2}) \quad \text{--- (2)}$$


i is max when $\sin(\omega t - \frac{\pi}{2}) = 1$

$$\therefore I_m = \frac{V_m}{\omega L}$$

$$\therefore i = I_m \sin(\omega t - \frac{\pi}{2}) \quad \text{--- (3)}$$

Phase angle and power factor:-

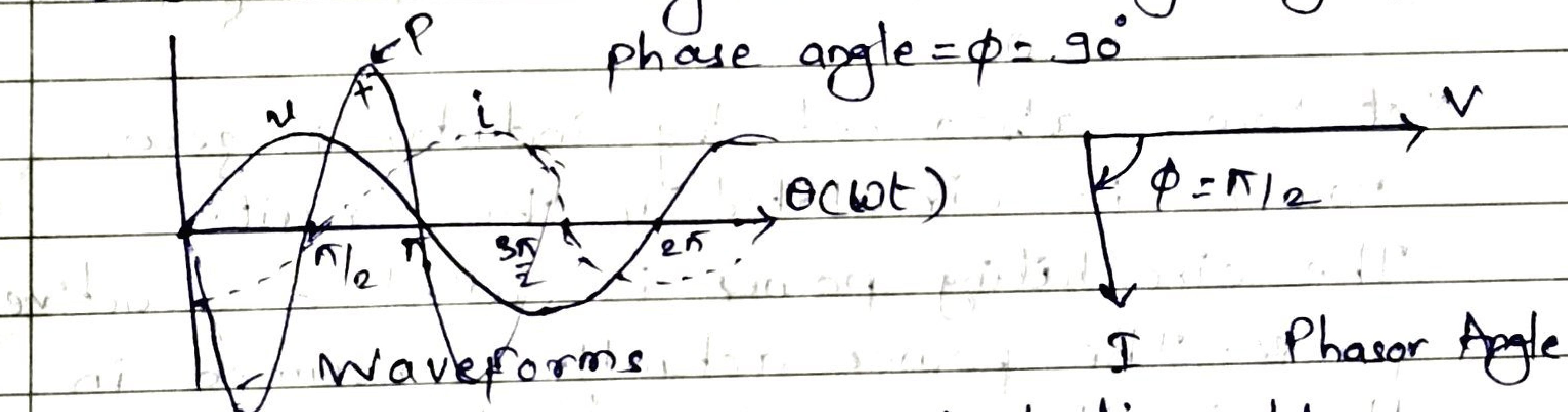From eq's (1), (2) and (3) it is observed that the current lags behind voltage by $\pi/2$ or 90°



Power factor of pure inductive circuit

$$PF = \cos\phi = \cos 90^\circ = 0 \text{ Lagging}$$

Impedance (Z)

$$I_m = \frac{V_m}{\omega L} \quad \text{or} \quad \omega L = \frac{V_m}{I_m}$$

$$\frac{\frac{V_m}{\sqrt{2}}}{\frac{I_m}{\sqrt{2}}} = \omega L$$

$$\therefore \frac{V}{I} = \omega L$$

$$\therefore \frac{V}{I} = Z = \omega L$$

ωL is called as inductive reactance X_L

of coil. $\therefore X_L = \omega L \Omega$

$$X_L = 2\pi f L \Omega$$

Power :- Instantaneous power.

$$P = VI$$

$$= V_m \sin \omega t \times I_m \sin \left(\omega t - \frac{\pi}{2} \right)$$

$$= -V_m I_m \sin \omega t \cos \omega t$$

$$= -\frac{1}{2} V_m I_m \sin 2\omega t$$

Since power is² a scalar quantity, avg. power over a complete cycle to be considered.

∴ Average power = $P = \text{Average of } P \text{ over one cycle.}$


$$P = \frac{1}{2\pi} \int_0^{2\pi} P d\omega t$$
$$= \frac{1}{2\pi} \int_0^{2\pi} -\frac{1}{2} V_m I_m \sin 2\omega t d\omega t$$
$$= 0$$

Net Power absorbed by inductor is zero.

Power is circulated in the circuit.

The circulating power is called as reactive power. The power actually consumed in the circuit is called as active power.

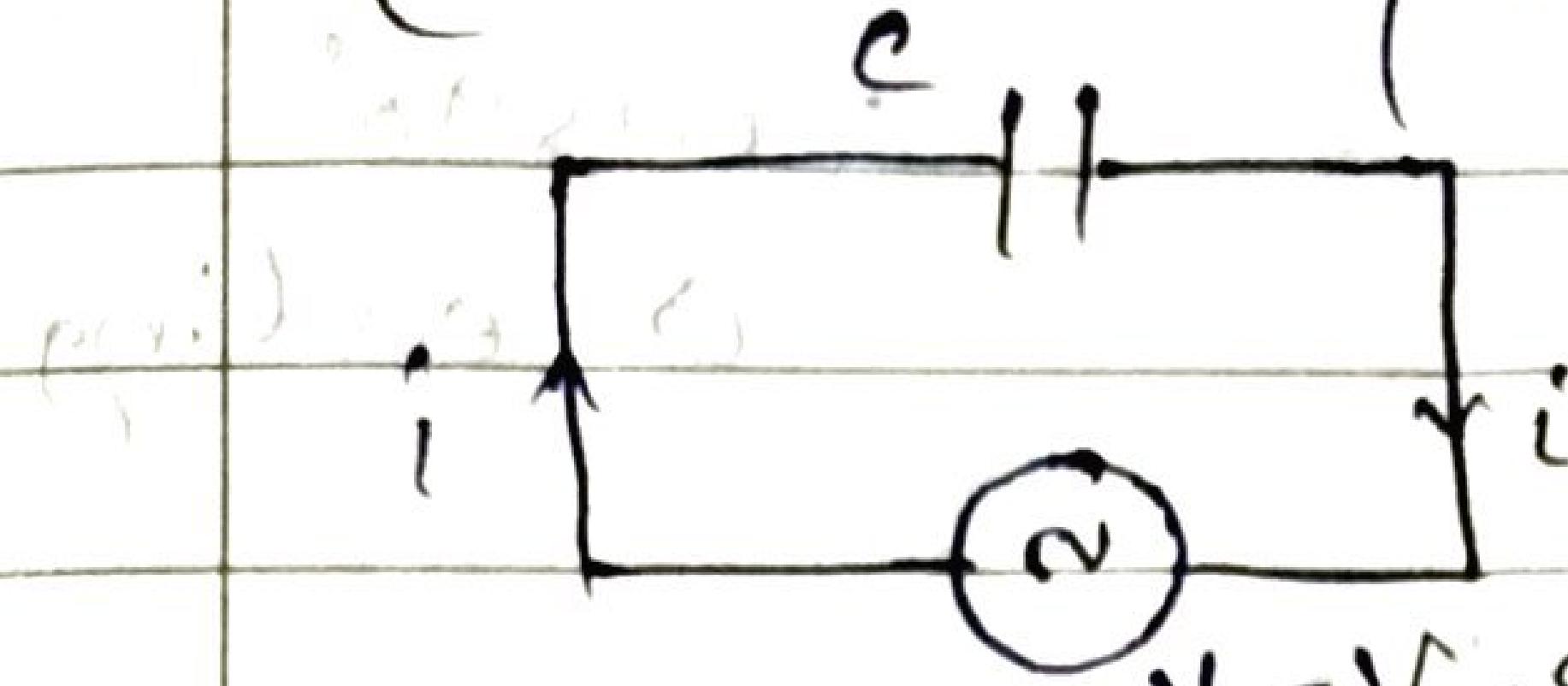AC Circuit Containing Pure Capacitance only (Pure Capacitive Circuit)



- Applied voltage

$$v = V_m \sin \omega t \quad \text{--- (1)}$$

Due to this alternating voltage alternating current i will flow through the circuit.

- charge on capacitor $q = CV$

Circuit current $i = \frac{dq}{dt}$ rate of change of charge

$$= \frac{dCV}{dt}$$

$$= \frac{d}{dt}(CV_m \sin \omega t)$$

$$= \omega CV_m \cos \omega t$$

$$\text{or } i = \omega CV_m \sin\left(\omega t + \frac{\pi}{2}\right)$$

value of i will be max. i.e. I_m when

$$\sin\left(\omega t + \frac{\pi}{2}\right) = 1$$

$$\text{so } I_m = \omega CV_m$$


$$\therefore [i = I_m \sin\left(\omega t + \frac{\pi}{2}\right)] \quad \text{--- (2)}$$

Phase angle and power factor:

From eq's (1) and (2) we get

the current leads the voltage by $\pi/2$ or 90° .

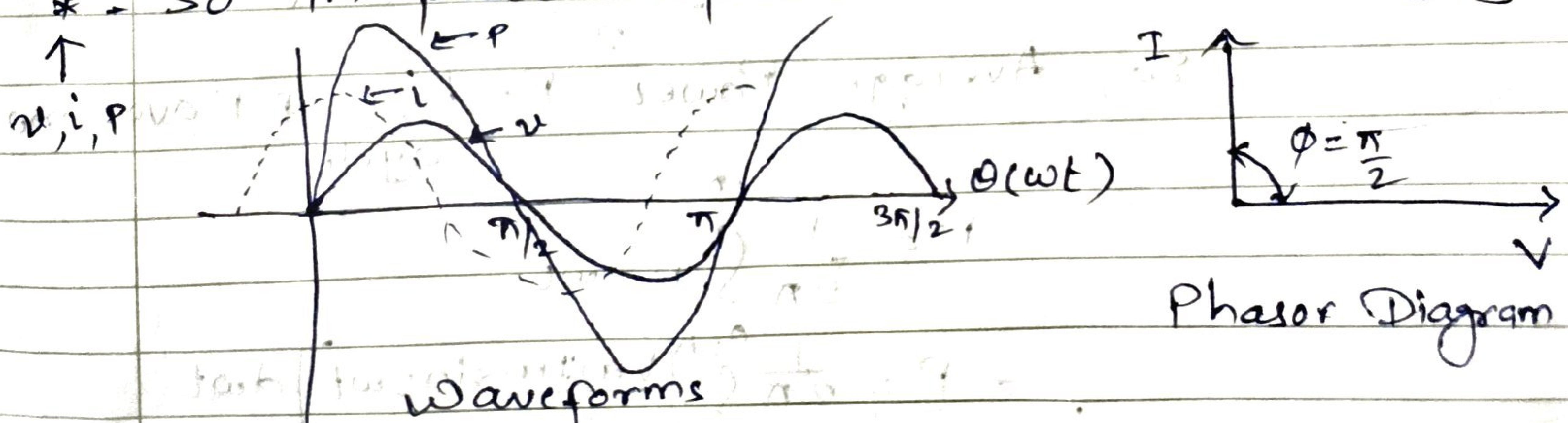* - So in pure capacitor current leads volg. by 90°



- phase angle of the circuit $\phi = 90^\circ$
- Power factor of the circuit, $PF = \cos\phi$
 $\therefore PF = \cos 90^\circ$
 $= 0$ Leading.

Opposition to current (Z)
we have: $I_m = \omega C V_m$

$$\frac{V_m}{I_m} = \frac{1}{\omega C}$$

Dividing both numerator and denominator by $\sqrt{2}$ for rms value

$$\frac{V_m/\sqrt{2}}{I_m/\sqrt{2}} = \frac{1}{\omega C}$$

$$\frac{V}{I} = \frac{1}{\omega C}$$

$$\therefore Z = \frac{1}{\omega C}$$

This is called as capacitive reactance X_C of the capacitor.

$$\therefore X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

Power (P) :- Instantaneous power $p = VI$

$$= V_m \sin \omega t \times I_m \sin(\omega t + \frac{\pi}{2})$$

$$= V_m I_m \sin \omega t \cos \omega t$$

$$= \frac{V_m I_m}{2} \sin 2\omega t$$

So, Average Power $P = \text{Avg. of } p \text{ over one cycle}$

$$P = \frac{1}{2\pi} \int_0^{2\pi} p d\omega t$$

$$= P = \frac{1}{2\pi} \int_0^{2\pi} [V_m I_m \sin 2\omega t] d\omega t$$

* Power absorbed in pure capacitance is zero.

Sums on pure L and C

① A 10mH inductor has current of $i = 5\cos(2000t)$. Obtain the volg. V_L across it.

Soln. $L = 10\text{mH} = 10 \times 10^{-3}\text{H}$, $i = 5\cos(2000t)$
we can write eqⁿ as foll.

$$i = 5\sin(2000t + \frac{\pi}{2})$$

$$\omega = 2000 \text{ rad/sec.} \quad \phi = \frac{\pi}{2} \text{ rad} = 90^\circ$$

$$\text{rms value of current } I = \frac{I_m}{\sqrt{2}} = \frac{5}{\sqrt{2}} = 3.54\text{A}$$

$$X_L = \omega L = 2000 \times 10 \times 10^{-3} = 20\Omega$$

$$\therefore V_L = IX_L = 3.54 \times 20 = 70.8\text{V}$$

Or

$$v_L = L \frac{di}{dt} \\ = 10 \times 10^{-3} \frac{d}{dt} [5\cos(2000t)]$$

$$= -10 \times 10^{-3} \times 5 \times 2000 \sin 2000t$$

$$\text{or } v_L = 100 \sin(2000t + 180^\circ)$$

$$\therefore V_m = 100\text{V.}$$

$$\therefore V_L = \frac{100}{\sqrt{2}} = 70.71\text{V}$$

2 A $318\mu\text{F}$ cap^r is connected across 230V, 50Hz system. Determine (i) capacitive reactance (ii) rms value of current and (iii) eq's for volg & current.

Soln. (i) Capacitive reactance $= X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 318 \times 10^{-6}}$

$$X_C = 10\Omega$$

$$(ii) \text{ Rms value of current} = I = \frac{V}{Z} = \frac{V}{X_C} = \frac{230}{10} = 23\text{Amp}$$

$$\text{iii) } V_m = \sqrt{2} \times V, \text{ in half wave rectifier} \\ = \sqrt{2} \times 230 \\ = 325.27 \text{ V}$$

$$I_m = \sqrt{2} \times I$$

$$= \sqrt{2} \times 23$$

$$= 32.53 \text{ A}$$

(from voltage & current eqns are)

$$v = 325.27 \sin(2\pi \times 50)t$$

$$= 325.27 \sin 314t$$

$$\text{or: } i = 32.53 \sin \left(314t + \frac{\pi}{2} \right)$$

$$325.27 \times 0.1201 \times 6000 = 100 \text{ mJ}$$

$$V_{3.0V} \text{ component is } 100 \text{ mV}$$

$$100 \text{ mV} = 0.1 \text{ V}$$

$$100 \text{ mV} = 100 \text{ mV}$$

$$(0.001 \text{ A}) \times 100 \text{ mV} = 100 \mu\text{A}$$

$$100 \mu\text{A} \times 1000 \times 1000 = 100 \text{ mA}$$

$$(0.001 \text{ A}) \times 1000 \times 1000 = 100 \text{ mA}$$

$$100 \mu\text{A} \times 1000 \times 1000 = 100 \text{ mA}$$

Candidate Roll No. _____

(In figures)

Name: _____

Test Exam. _____

Date: _____

Branch/Semester _____

Junior Supervisor's full
Signature with Date

Examination: _____

Subject: _____

Question No.	1	2	3	4	5	6	7	8	9	10	11	12	Total
Marks Obtained													

AC Series Circuits

Series ac circuit :-

A ckt in which the same alternating current flows through all the elements

R, L, C. Different types

1) R-L series ckt

2) R-C $+1-$ $+1-$

3) R-L-C $+1$ $-1-$

For these types study of foll is important:


1) phase angle ϕ bet' applied volg & current

2). nature of the circuit (whether resistive, inductive or capacitive)

3) Circuit impedance

4) Power consumed

1) R-L series circuit:-

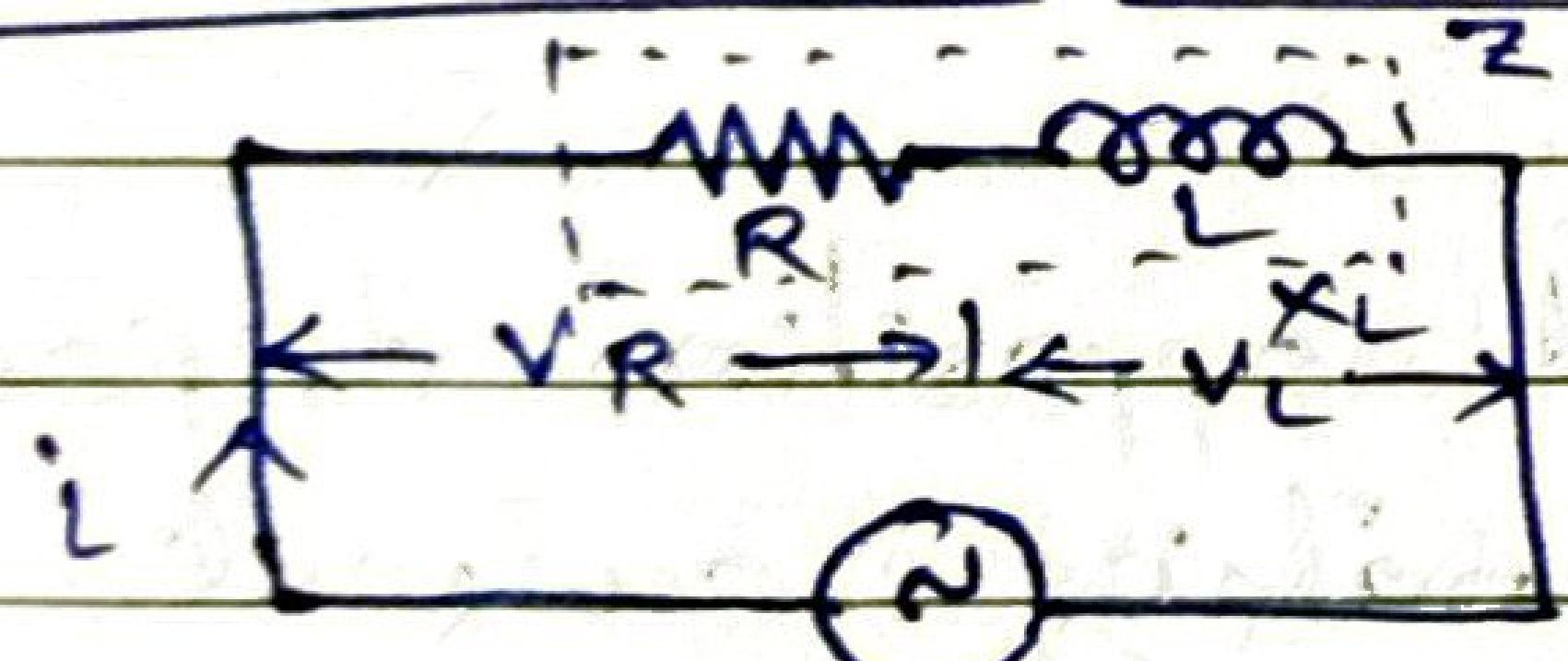

V = rms value of applied

volg.

I = rms. value of current

Z = impedance of the circuit

As per Ohm's law


$$V_R = IR \quad \rightarrow \quad V_R \text{ in phase with } I$$

$$V_L = IX_L \quad \rightarrow \quad V_L \text{ leads } I \text{ by } 90^\circ$$


$$V = IZ$$

Phasor diagram:-

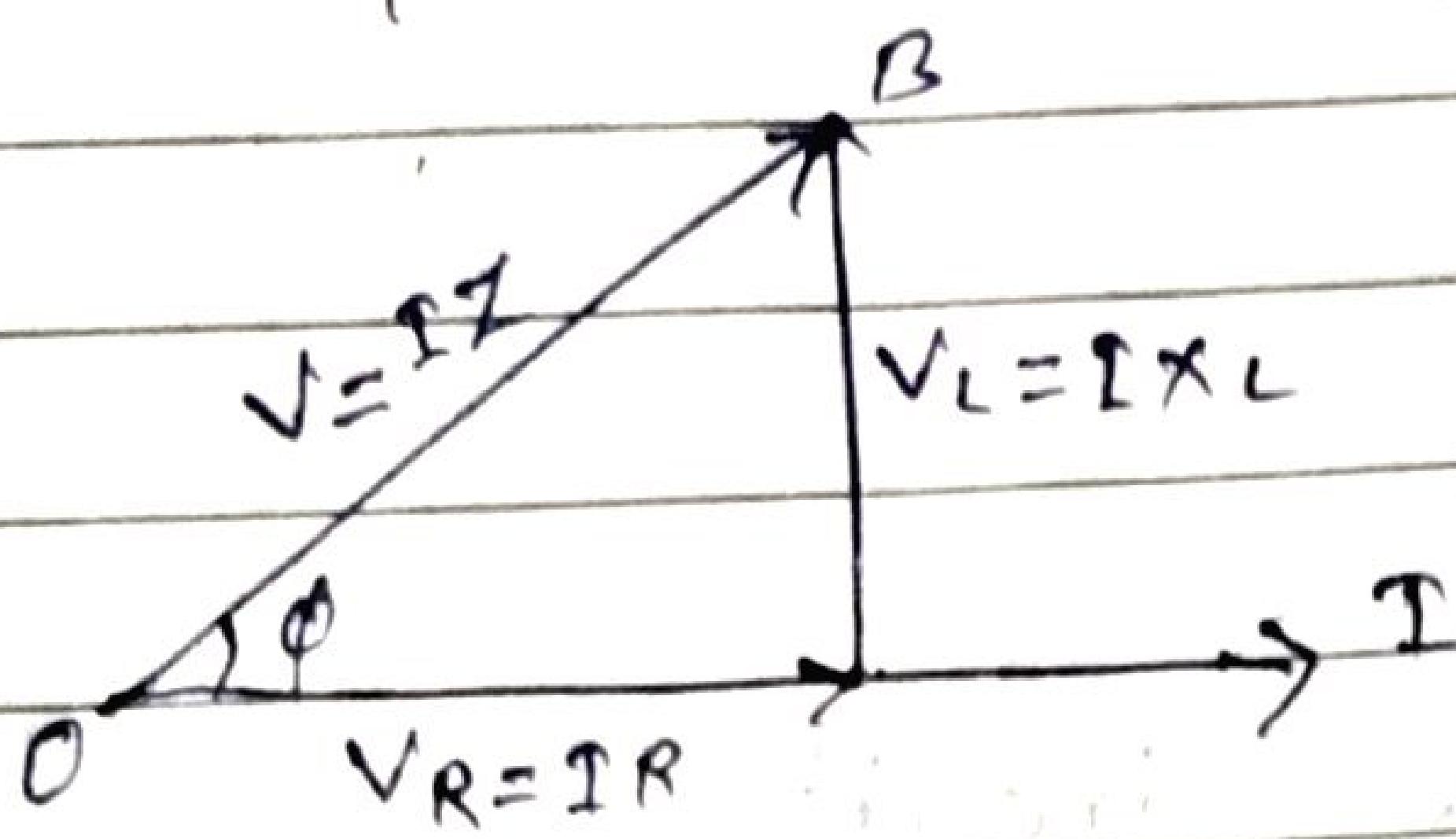Taking current as the reference phasor, the phasor dia. of the ckt will be



Phasor dia.

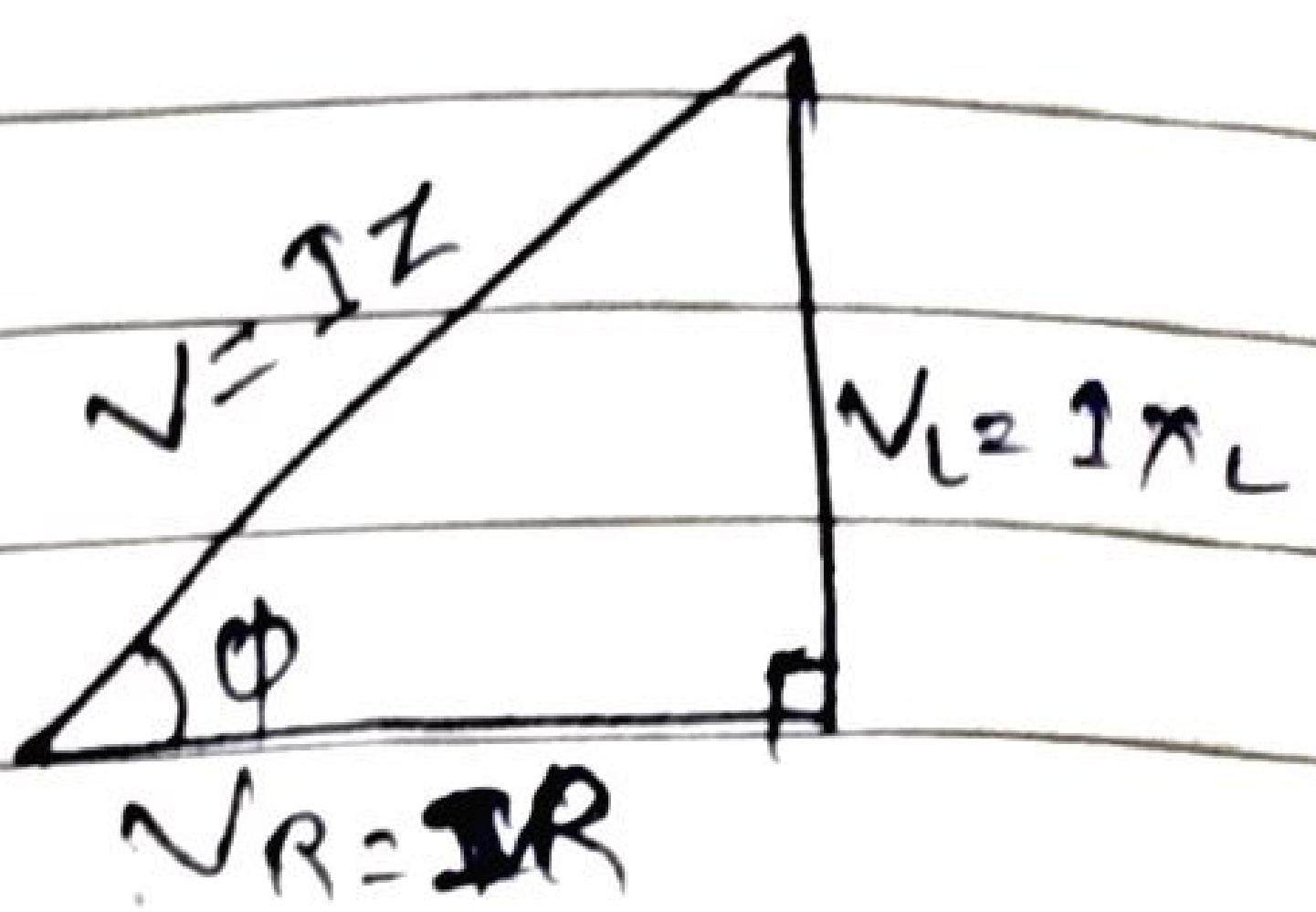

voltage triangle

w.r.t. the ckt dia. volg. eq:

$$\bar{V} = \bar{V}_R + \bar{V}_L$$

$$\text{phase angle of ckt } \phi = \tan^{-1} \frac{V_L}{V_R} = \tan^{-1} \frac{I X_L}{I R}$$

$$\text{Power factor of ckt } PF = \cos \phi = \frac{V_R}{V} = \frac{IR}{\sqrt{R^2 + X_L^2}}$$


$$PF = \frac{R}{Z} \text{ lagging}$$

Ckt current I lags behind applied volg. nature of power factor is lagging.

Voltage triangle:- The voltage along with its components can be represented by a right-angled triangle known as voltage triangle.

Impedance Z :- Total opposition offered to the flow of alternating current.

Impedance has two components

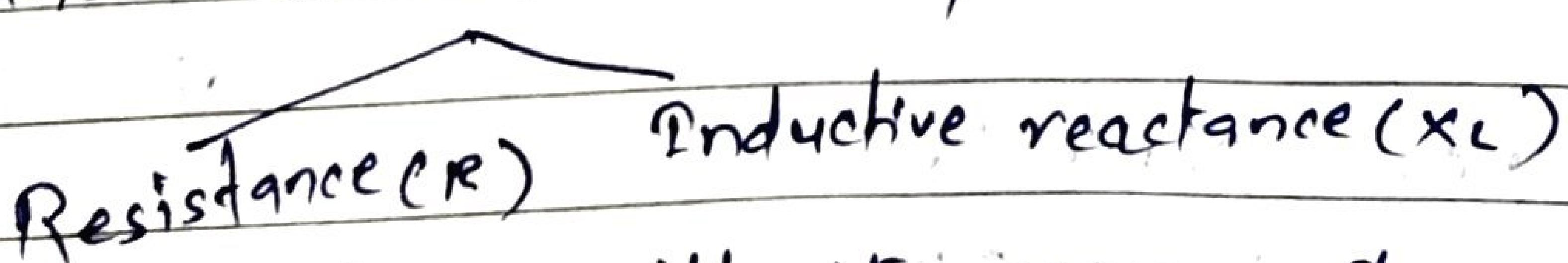

Impedance along with its components can be represented by right-angled triangle known as impedance triangle.



Impedance Triangle

From impedance triangle,

$$\text{Impedance } Z = \sqrt{R^2 + X_L^2} \Omega$$

In rectangular form Z is expressed as:

$$Z = (R + jX_L) \Omega \rightarrow \text{rect. form}$$

In polar form

$$Z = (Z \angle \phi) \Omega$$

Power P


- Power consumed in the ckt is called active or true power (in case of R)
- Circulating power is called reactive power (in case of L or C).

Active power = $P = \text{Voltage} \times \text{Current in phase with voltage}$

Reactive power = $Q = \text{voltage} \times \text{current } 90^\circ \text{ out of phase with voleg.}$

For R-L ckt

Taking V as reference phasor,

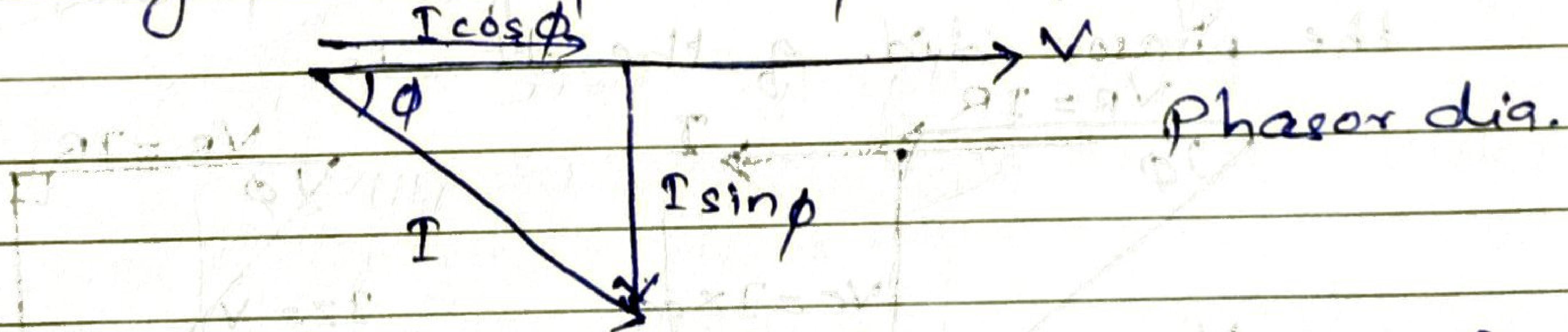

Current I is resolved in 2 components

- $I \cos \phi$ — in phase with voltage
- $I \sin \phi$ — 90° out of phase with voltage


Active power $P = VI \cos \phi$ Watts or kilowatt

Reactive Power $Q = VI \sin \phi$ VAR or kVAR

Apparent Power $S = VI$ VA or kVA

Power triangle:-

$$VI \cos\phi = P$$

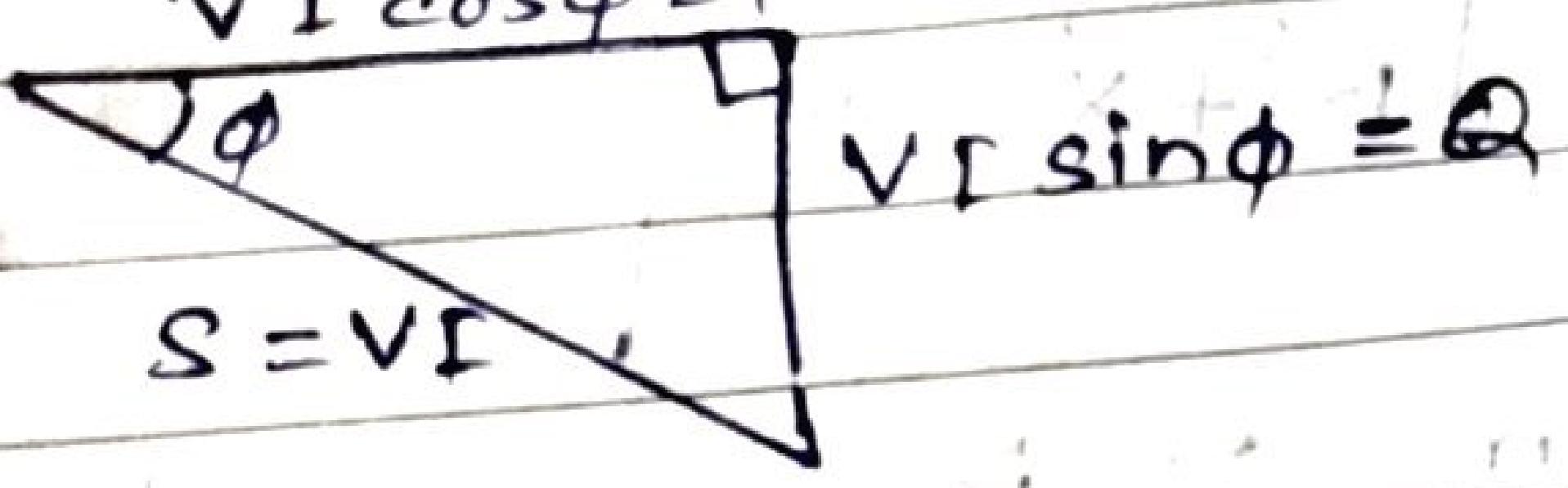


from power triangle

$$(Active\ power)^2 + (Reactive\ power)^2 = (Apparent\ power)^2$$

$$P^2 + Q^2 = S^2$$

R - C series circuit

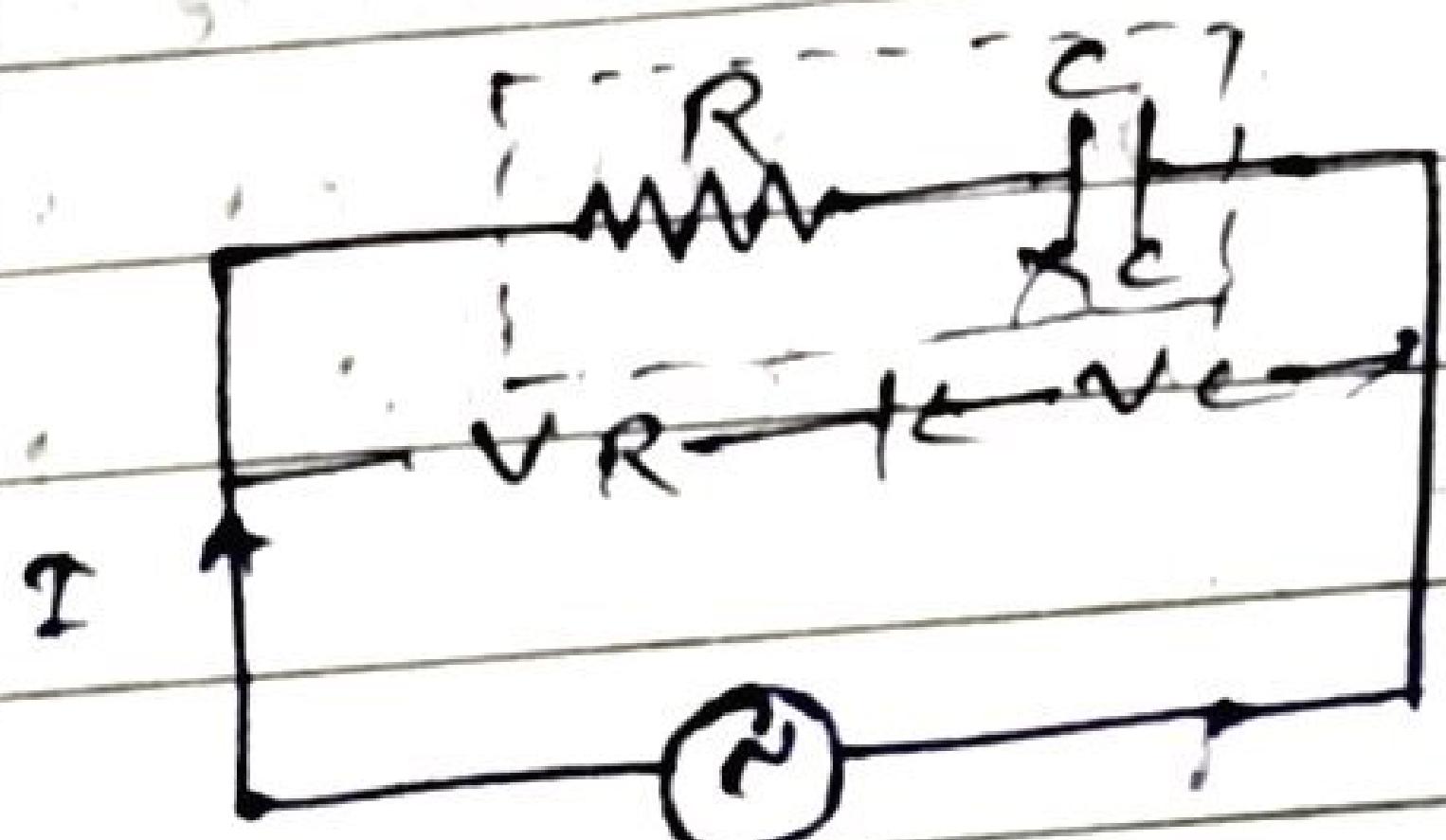

V = rms value of applied volg.

I = rms value of ckt current

Z = impedance of the ckt

By Ohm's law

$$VR = IR \rightarrow VR \text{ is phase } I$$

$$VC = IX_C \rightarrow VC \text{ lags behind } I \text{ by } 90^\circ$$

$$V = IZ$$

Phasor Dia.

Taking current as the reference phasor,

the phasor dia. of the ckt is

$$VR = IR$$

$$V = IZ$$

$$VC = IX_C$$

$$VR = IR$$

$$IZ = V$$

$$VC = IX_C$$

voltage Triangle

$$\bar{V} = \bar{V}_R + \bar{V}_C$$


Current I leads the applied volg. V by ϕ .
($\phi \leq 90^\circ$): Nature of ckt is capacitive.

$$\phi = \tan^{-1} \frac{V_C}{V_R} = \tan^{-1} \frac{X_C}{R}$$

Power factor of the ckt $\text{pf} = \cos\phi = \frac{V_R}{V} = \frac{IR}{IZ}$

As current I leads applied volg. nature
of power factor is leading.

Impedance (Z)

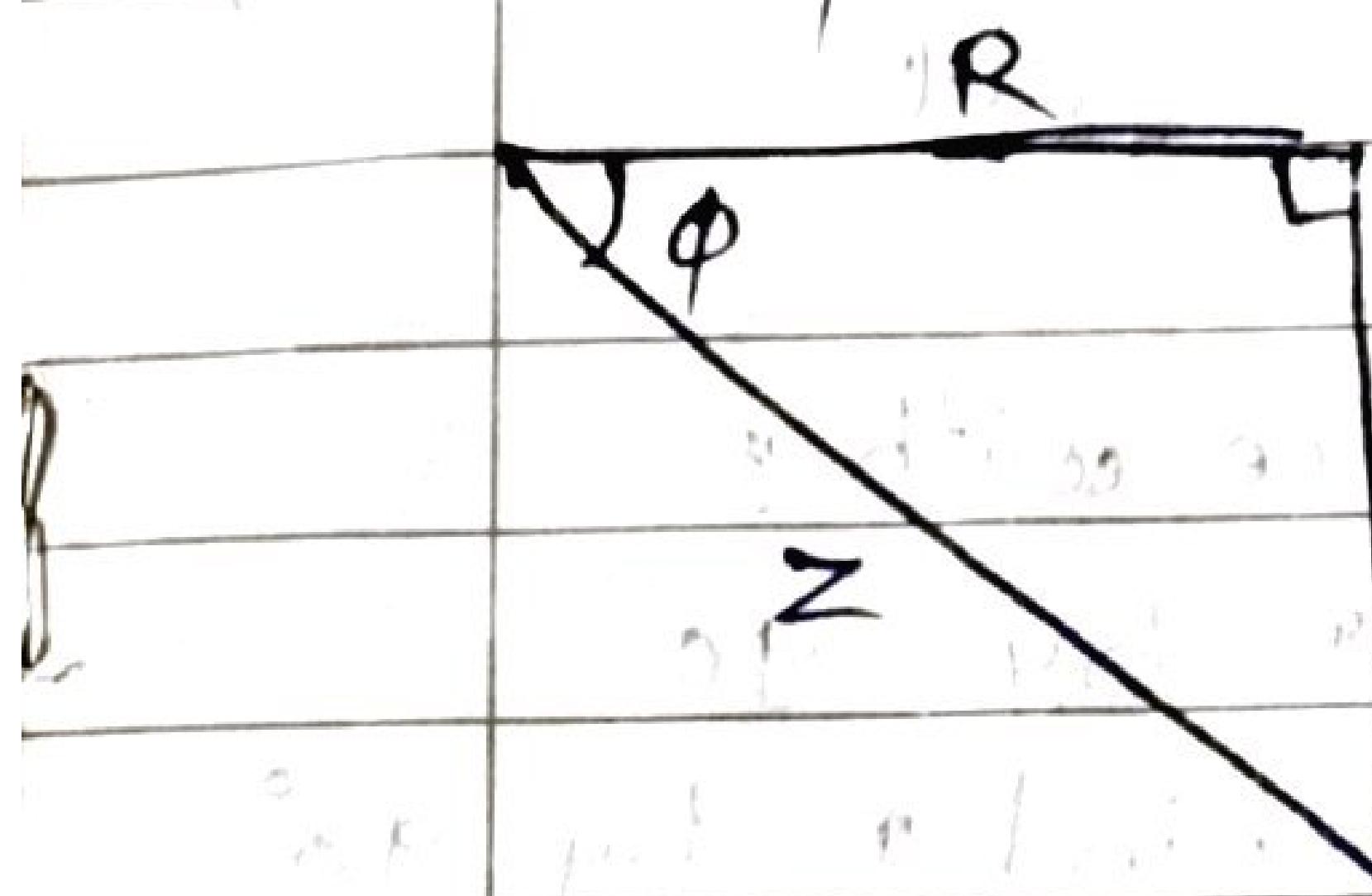

Impedance Triangle

Dividing each of volg. phasor by I in a volg. triangle we get the impedance triangle.

Circuit impedance


$$Z = \sqrt{R^2 + X_c^2} \Omega$$

$$Z = (R - jX_c) \Omega$$

$$\bar{Z} = (Z \angle -\phi) \Omega$$

Power (P)

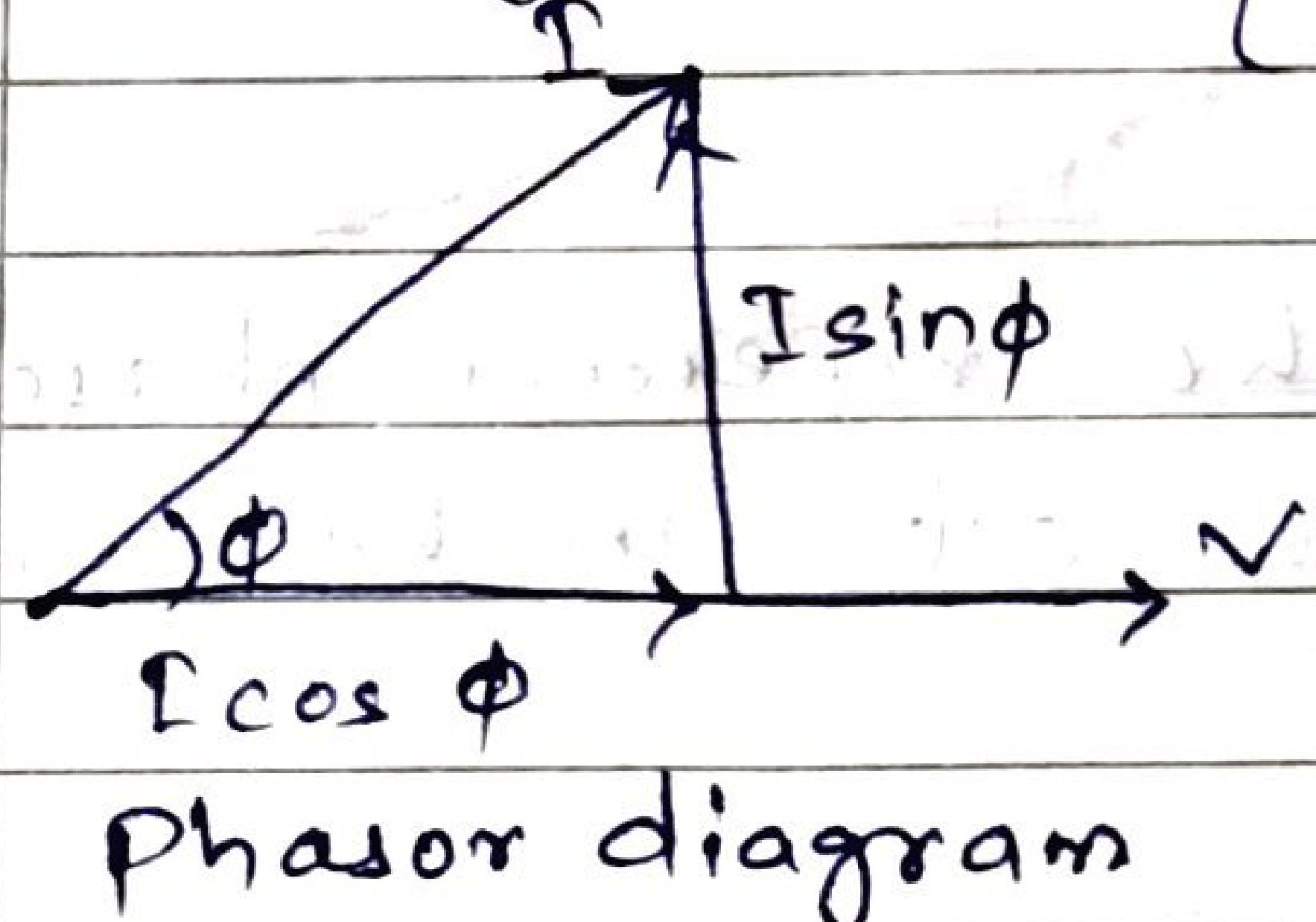Taking V as reference phasor dia. will be
(only volg + current phasor are drawn)



Phasor diagram

Circuit current can be resolved into two components
 i) $I \cos\phi$ — in phase with V
 ii) $I \sin\phi$, — 90° out of phase with Voltage

Multiplying each of current phasor by V in above dia. we get power triangle as:

$$S = VI \text{ (Apparent power)}^2$$

(kVA)

$$Q = VI \sin\phi \text{ (kVAR)}$$

(Active power)² +

(Reactive power)²


$$P = VI \cos\phi \text{ (kW)}$$

$$S^2 = P^2 + Q^2$$

Power triangle

$$\text{So power factor } \text{pf} = \cos\phi = \frac{P}{S}$$

R-L-C Series Circuit

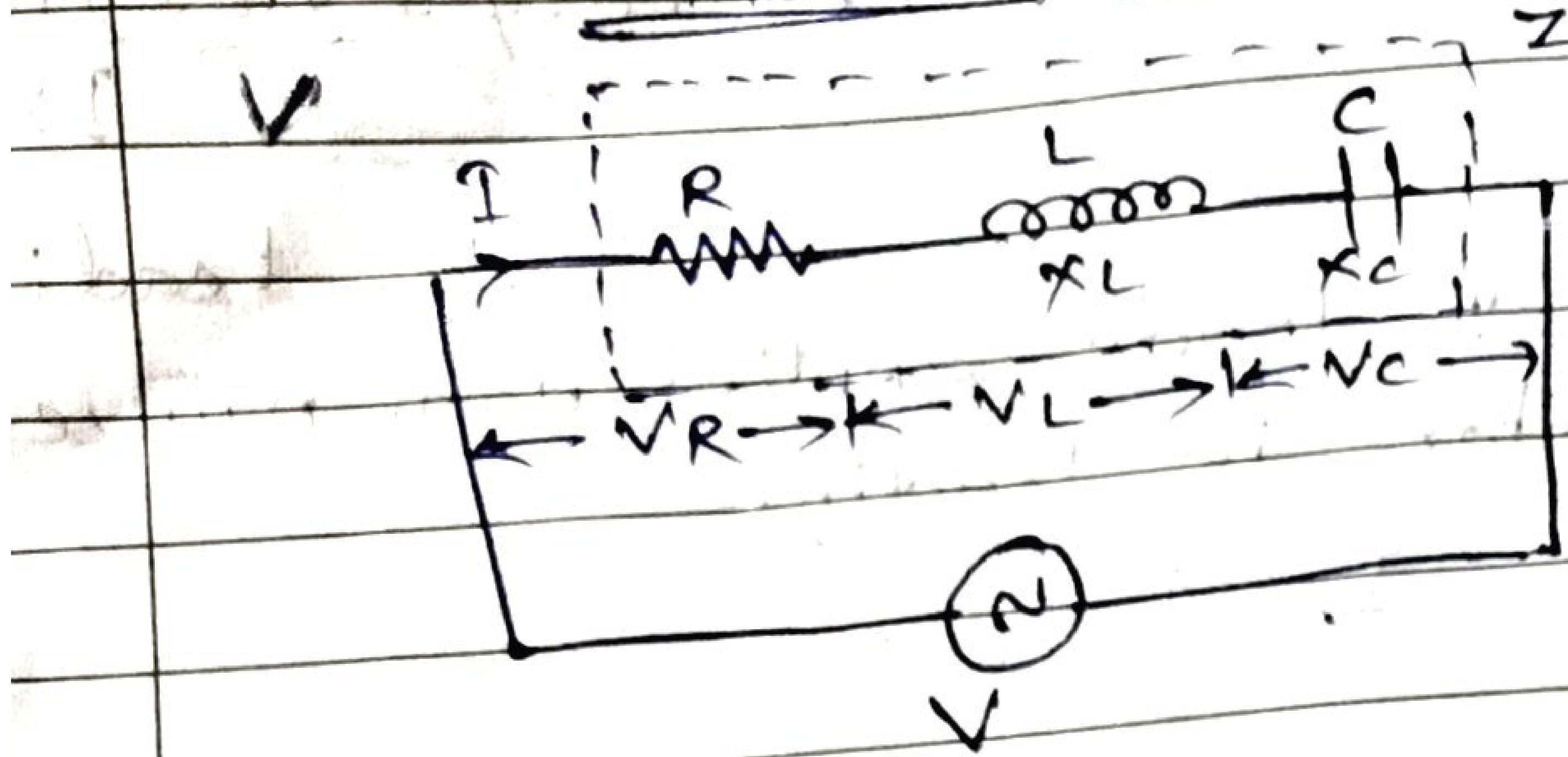

V = rms value of applied volg.

I = rms value of circuit current

Z = impedance of ckt

By Ohm's law

$$V_R = I R \quad \text{--- } V_R \text{ in phase with } I$$

$$V_L = I X_L \quad \text{--- } V_L \text{ leads } I \text{ by } 90^\circ$$

$$V_C = I X_C \quad \text{--- } V_C \text{ lags behind } I \text{ by } 90^\circ$$

$$V = IZ$$


R-L-C series ckt can be effectively inductive, capacitive or resistive that depends on values of X_L and X_C .

case ① $X_L > X_C$

If $X_L > X_C$ then $V_L > V_C$, capacitive effect gets neutralized and the circuit behaves like R-L ckt.

Phasor diagram:-

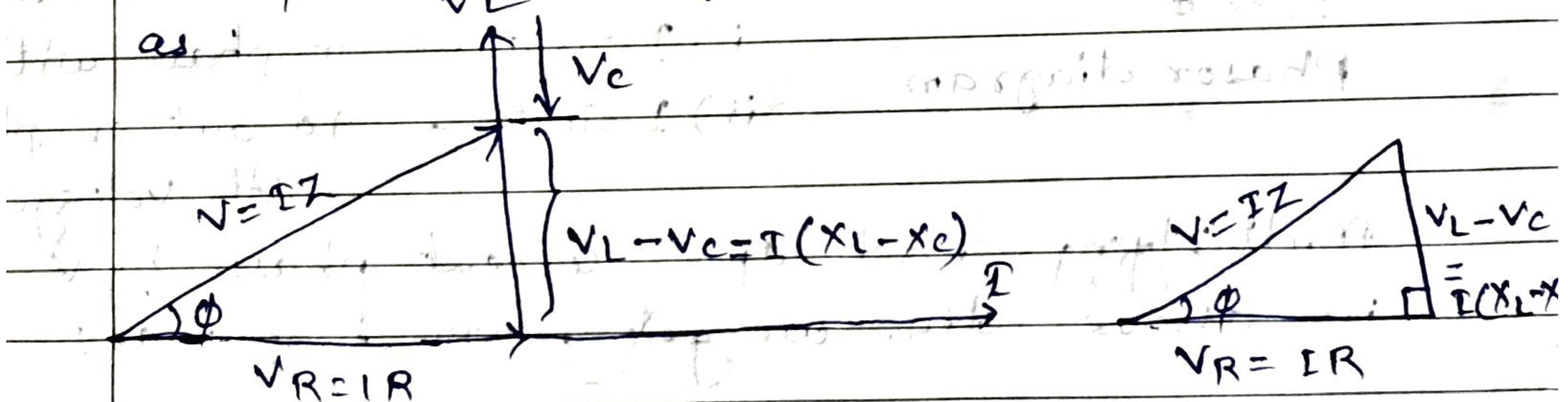Taking current as the reference phasor, the phasor dia. of the ckt can be drawn as:



Phasor Diagram

Voltage triangle

From the ckt dia.

$$\bar{V} = \bar{V}_R + \bar{V}_L + \bar{V}_C$$

- From phasor dia. it is clear that the current I lags behind the applied voltage V by ϕ^o ($\phi \geq 90^o$).
- So, the nature of the circuit is inductive.


- Phase angle of the circuit

$$\begin{aligned}\phi &= \tan^{-1} \frac{V_L - V_C}{V_R} = \tan^{-1} \frac{I(X_L - X_C)}{I R} \\ &= \tan^{-1} \left[\frac{(X_L - X_C)}{R} \right]\end{aligned}$$

So power factor of the circuit

$$PF = \cos \phi = \frac{V_R}{V} = \frac{IR}{IZ} = \frac{R}{Z} \text{ lagging}$$

Impedance (Z)

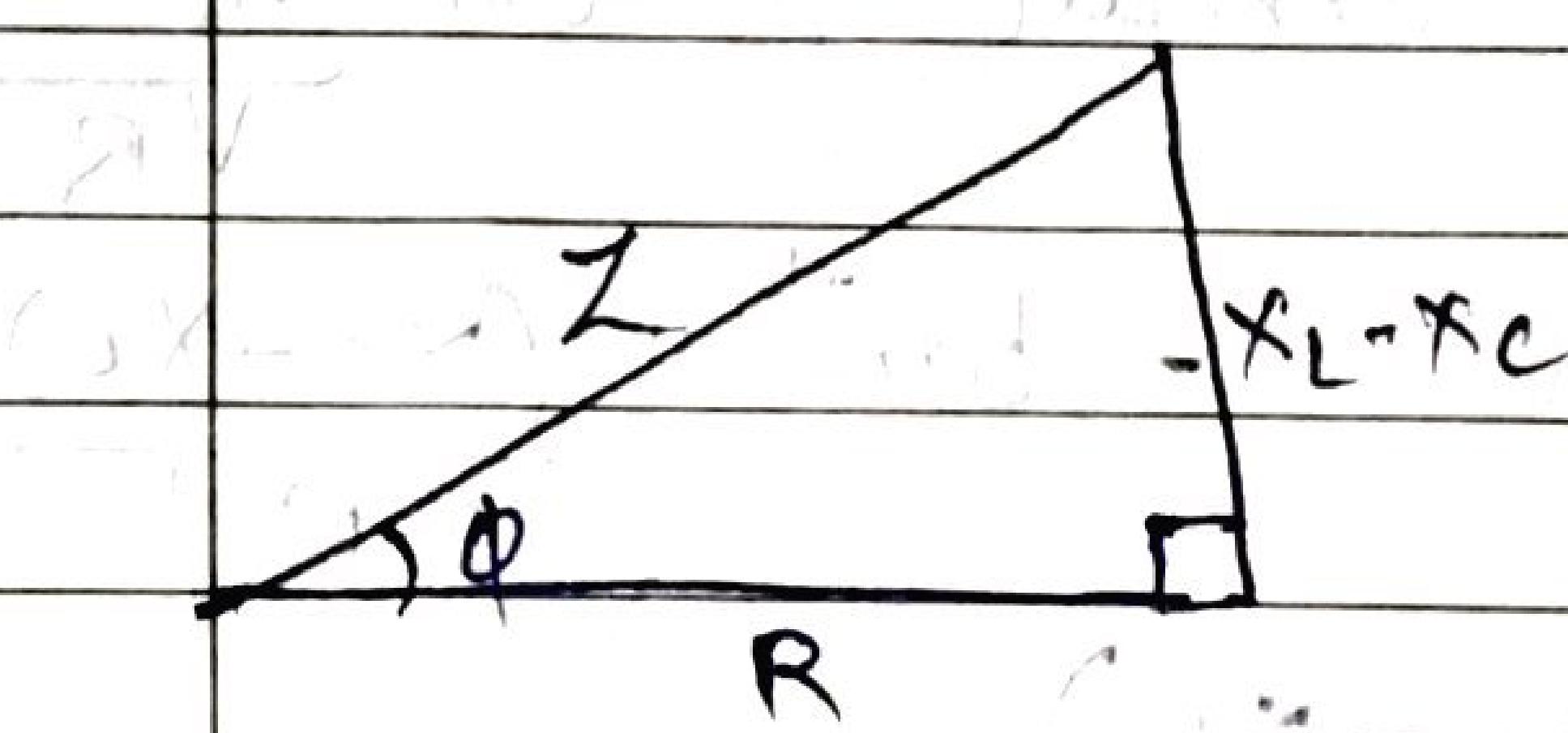

- Dividing each of voltage phasor by I in voltage triangle we get impedance triangle as shown.

Impedance Triangle
(when $X_L > X_C$)

$$\text{from impedance triangle } Z = \sqrt{R^2 + (X_L - X_C)^2} \Omega$$

Impedance in rectangular form

$$\bar{Z} = R + j(X_L - X_C) \Omega$$


Impedance in polar form

$$\bar{Z} = (Z \angle \phi) \Omega$$

Case ② $X_C > X_L$

- If $X_C > X_L$, then inductive effect get neutralized and the circuit behaves like a R-C circuit.

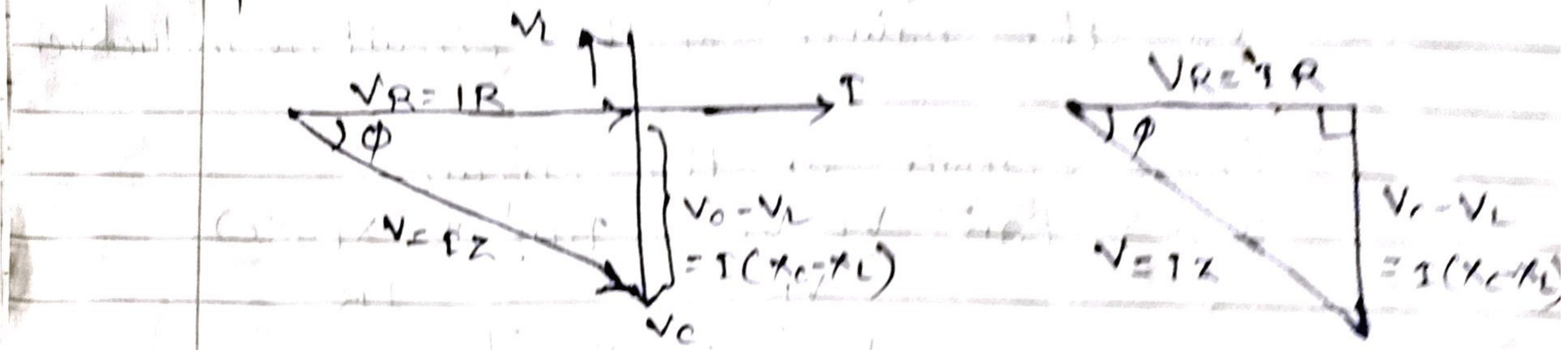Phasor Diagram :- taking current I as reference phasor, phasor dia. will be as shown



Phasor diagram

Voltage Triangle

- Current I leads the applied voltage V by ϕ° ($\phi^{\circ} < 90^{\circ}$), so, nature of the ct is capacitive.


- Phase angle of the circuit $\phi = \tan^{-1} \frac{V_c - V_L}{V_R}$

$$\begin{aligned} \phi &= \tan^{-1} \frac{I(X_C - X_L)}{I R} \\ &= \tan^{-1} \left(\frac{X_C - X_L}{R} \right) \end{aligned}$$

- Power factor of the circuit

$$PF = \cos \phi = \frac{V_R}{V} = \frac{IR}{IZ} = \frac{R}{Z} \text{ leading}$$

Impedance (Z)

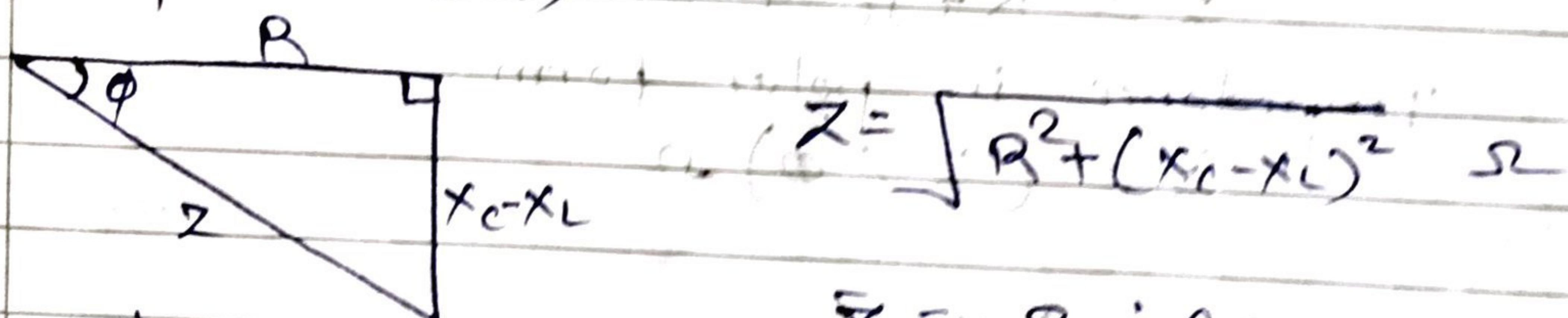

$$Z = \sqrt{R^2 + (X_C - X_L)^2} \Omega$$

Impedance
Triangle ($X_C > X_L$)

$$Z = \sqrt{R^2 + j(X_C - X_L)^2} \Omega$$

Name:	Candidate Roll No. _____	Date _____
		(In figures) _____
Date:	20/11/2018	Test Exam.
Examination:	Branch/Semester	Junior Supervisor's full Signature with Date
Subject:		

Question No.	1	2	3	4	5	6	7	8	9	10	11	12	Total
Marks Obtained													

1

A coil having a resistance of 7Ω and inductance of 31.8 mH is connected to $230V, 50\text{Hz}$ supply.

Calculate: ① Circuit current
② phase angle ③ power factor ④ power consumed

Sol:

$$\text{Inductive reactance } X_L = 2\pi f L$$

$$= 2\pi \times 50 \times 31.8 \times 10^{-3}$$

$$= 10\Omega$$

$$\text{Impedance of coil, } Z_{\text{coil}} = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{(7)^2 + (10)^2}$$

$$Z_{\text{coil}} = 12.21\Omega$$

① Using Ohm's law

$$\text{Circuit current } I = \frac{V}{Z_{\text{coil}}} = \frac{230}{12.21}$$

$$I = 18.84 \text{ Amp}$$

② Phase angle $\phi = \tan^{-1} \frac{X_L}{R} = \tan^{-1} \frac{10}{7}$

$$\phi = 55^\circ$$

③ Power Factor, $PF = \cos \phi = \cos 55^\circ$


= 0.574 lagging

(current is inductive)

④ Power consumed $P = IV \cos \phi$

$$= 230 \times 18.84 \times 0.574$$

$$P = 2487.26 \text{ W}$$

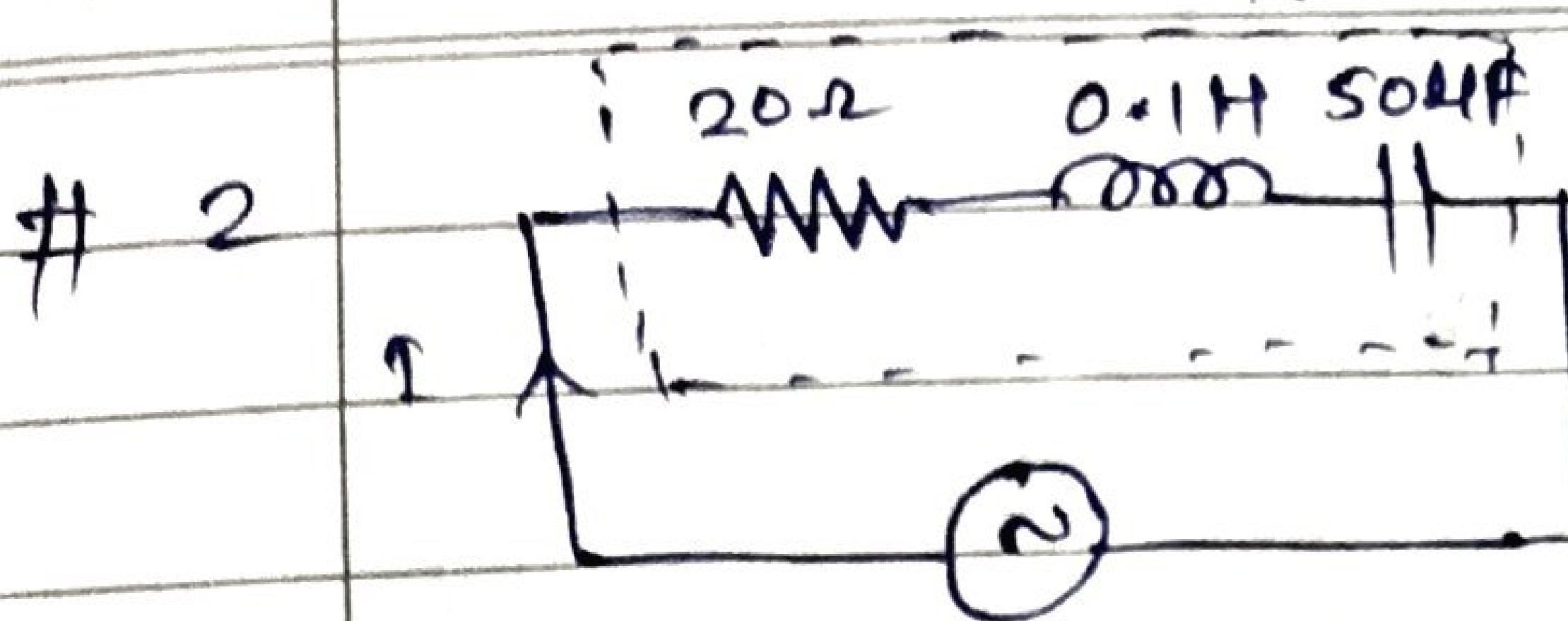

$V = 200V, 50\text{Hz}$

For the given circuit
determine

- (1) Circuit impedance
- (2) Circuit current
- (3) Power factor
- (4) Active Power
- (5) Reactive Power
- (6) Apparent Power

Soln. Total reactance $= X = X_C - X_L$ ($X_C > X_L$)

$$X_L = 2\pi fL = 2\pi \times 50 \times 0.1 = 31.42 \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 50 \times 10^{-6}} = 63.66 \Omega$$

As $X_C > X_L$ circuit is capacitive

& Total reactance $X = X_C - X_L$

$$= (63.66) - (31.42)$$

$$\boxed{X = 32.24 \Omega}$$

Applied volg $\bar{V} = 200\angle 0^\circ V$

$$\bar{Z} = R - jX$$

$$= (20 - j32.24) \Omega$$

$$\text{or } \bar{Z} = Z \angle \phi$$

$$\phi = \tan^{-1} \left(\frac{X_C - X_L}{R} \right)$$

(1)

$$= (37.94 \angle -58.19) \Omega = -58.19$$

$$Z = \sqrt{R^2 + (X_C - X_L)^2} \therefore Z = 37.94 \Omega$$

(2) Circuit current $\bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{200\angle 0^\circ}{(37.94 \angle -58.19)}$
 $\therefore I = 5.27 \angle 58.19^\circ \text{ Amp}$

(3) Power factor $PF = \cos \phi$

$$= \cos(-58.19^\circ)$$

= 0.527 leading

As $X_C > X_L$ ckt is capacitive \therefore leading PF.

(4)

Active Power $= P = VI \cos \phi$

$$= 200 \times 5.27 \times \cos(-58.19^\circ)$$

$$\boxed{P = 555.46 \text{ W}}$$

(5) Reactive power = $Q = VI \sin \phi$


$$= 200 \times 5.27 \times \sin(-58.19^\circ)$$

$$\boxed{Q = -895.69 \text{ VAR}}$$

(6) Apparent Power = $S = VI$

$$= 200 \times 5.27$$

$$\boxed{S = 1054 \text{ VA}}$$

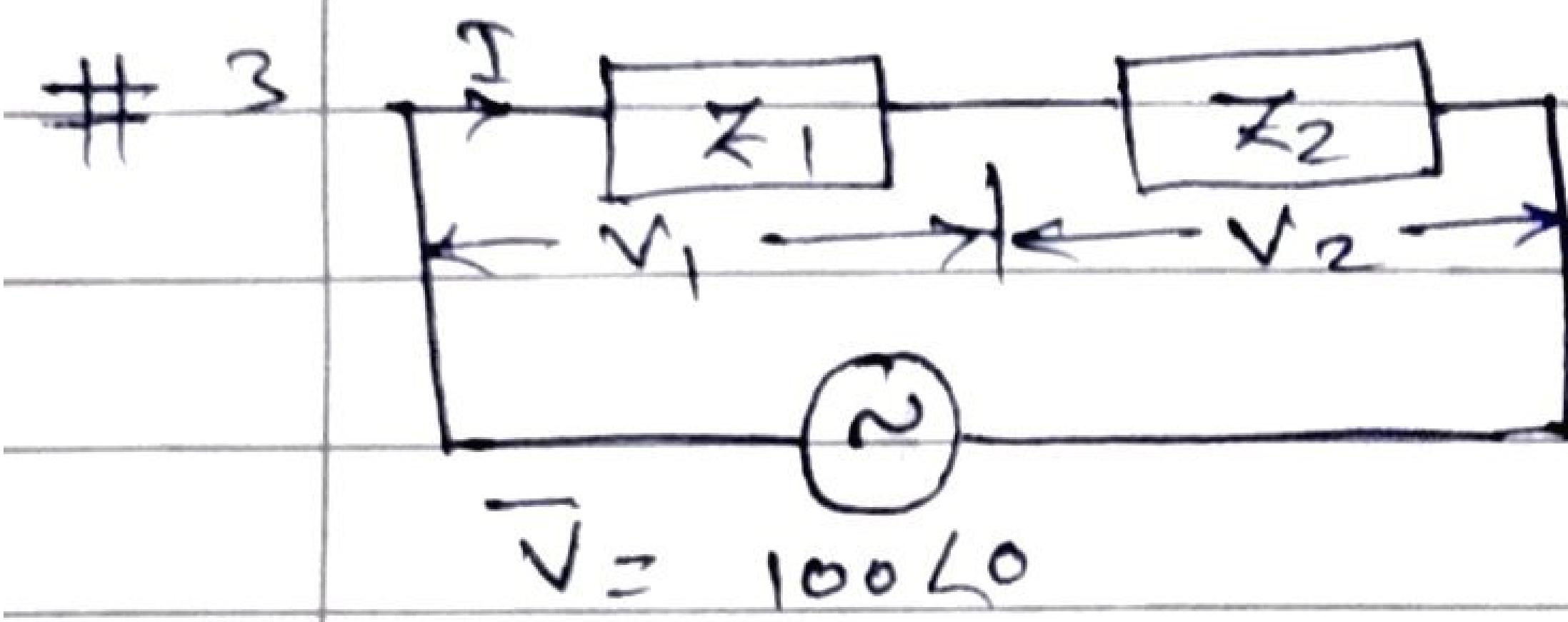

Rms volg. of 100L0 volts is applied to series combination of Z_1 and Z_2 where $\bar{Z}_1 = 20L30^\circ \Omega$.

The effective volg. drop across Z_1 is known to be $(40L-30^\circ)$ Volts.

Find the reactive component of Z_2 .

Sol.


$$\bar{Z}_2 = \frac{\bar{V}_2}{\bar{I}}$$

$$\begin{aligned}\bar{V}_2 &= \bar{V} - \bar{V}_1 = (100L0) - (40L-30) \\ &= (100+j0) - (34.64-j20) \\ &= (65.36+j20) \text{ Volts} \\ &= (68.35 L 17.01) \text{ Volts}\end{aligned}$$

$$\bar{I} = \frac{\bar{V}_1}{\bar{Z}_1} = \frac{(40L-30)}{(20L30)} = (2 L-60) \text{ Amp}$$

$$\begin{aligned}\bar{Z}_2 &= \frac{\bar{V}_2}{\bar{I}} = \frac{68.35 L 17.01}{2 L-60} \\ &= (34.175 L 77.01) \Omega \\ &= (7.68 + j33.3) \Omega\end{aligned}$$

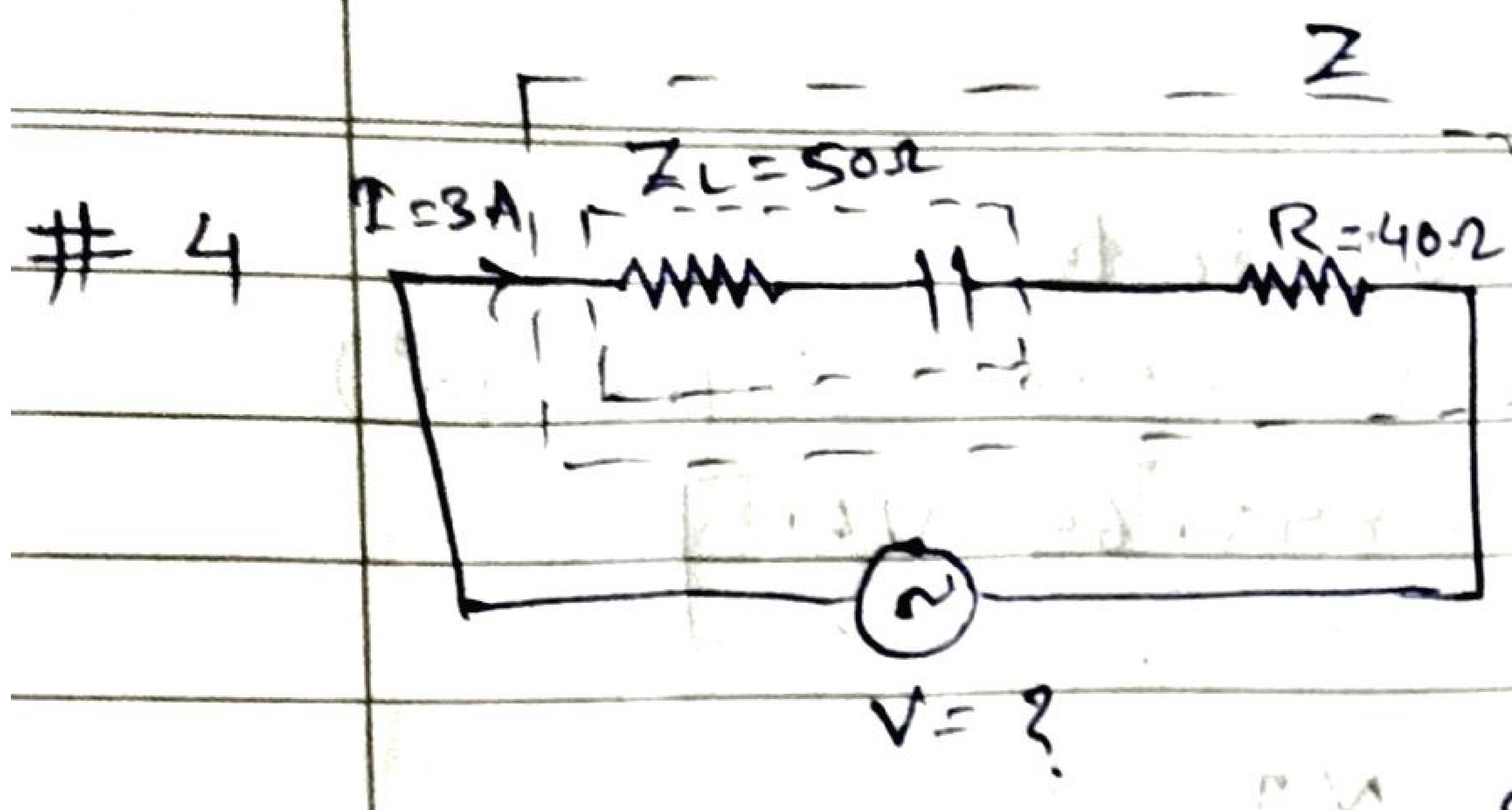$\boxed{\text{Reactive component of } Z_2 = 33.3 \Omega}$



A load consisting of a capacitor in series with a resistor has impedance of 50Ω and pf 0.707 leading. The load is connected in series with 40Ω res. across the supply and the resulting current is 3A. Determine the supply voltage and the overall phase angle.

Soln. PF = 0.707 Leading
 $\therefore \phi = 45^\circ$

$$\bar{Z}_L = 50 \angle -45^\circ \Omega$$

$$\bar{Z}_L = (35.36 - j35.36) \Omega$$

$$R \text{ of Load} = 35.36 \Omega$$

$$\text{Capacitive reactance of load} = 35.36 \Omega$$

$$\text{Total impedance of the circuit}$$

$$\begin{aligned}\bar{Z} &= [(35.36 + 40) - j35.36] \Omega \\ &= (75.36 - j35.36) \Omega\end{aligned}$$

$$\therefore \bar{Z} = (83.24 \angle -25.14^\circ) \Omega$$


The applied voltage is given by

$$\begin{aligned}\bar{V} &= I \bar{Z} = 3 \times 83.24 \\ &= 249.72 V\end{aligned}$$

$$\text{Overall phase angle} = 25.14^\circ$$

Resonance in AC circuits is the state of the ckt in which the inductive reactance of the ckt is equal to capacitive reactance.

Series Resonance:

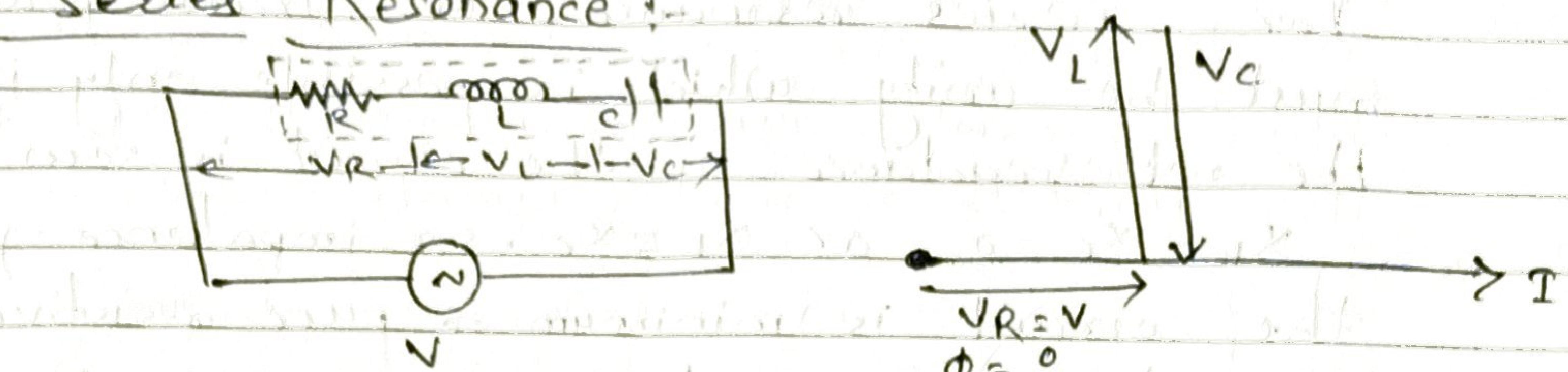

- In series R-L-C ckt

• When $x_L > x_C$, ckt is predominantly inductive total current lags behind applied volg.

• When $x_C > x_L$, ckt is predominantly capacitive total current leads applied volg.

Considering a series R-L-C ckt as shown in above dia.

Net reactance of the ckt is

$$X = (x_L - x_C) \Omega$$

where $x_L = 2\pi f L \Omega$

$$x_C = \frac{1}{2\pi f C} \Omega$$

At a certain supply freq. inductive reactance becomes equal to capacitive reactance, this freq. is called as resonant freq. fr.

Net reactance becomes zero. So impedance Z of the circuit behaves purely resistive ($Z = R$)

The whole circuit behaves as a purely resistive circuit and current remains in phase with the applied voltage ($\text{pf} = 1$). This condition is said to be the condition for electrical resonance.

Phasor diagram is shown for resonance condition.

ckt containing reactive elements (L and C) is resonant when ckt power factor is unity.

the applied voltage and current are in phase.

When this condition occurs in series R-L-C ckt, it is termed as Series resonance.

For series resonance, the circuit power must be unity which is possible only if the net reactance of the circuit is zero.

$X_L = X_C = 0$ or $X_L = X_C$. So impedance of the circuit is minimum & pure resistive. Current is max. at resonance. $I_r = \frac{V}{Z_r} = \frac{V}{R}$

As current is max. power absorbed by the circuit will also be at its max. value.

Volg. drop across L + C are very large. They are greater than the applied volg. But volg. drop across L-C combination will be zero because drops are equal in magnitude but 180° out of phase with each other.

Resonant Frequency :- (f_r)


- Series resonance at $X_L = X_C$

is achieved by changing supply freq. because $X_L = 2\pi f L$ & $X_C = \frac{1}{2\pi f C}$ are freq. dependent. The freq. at which $X_L = X_C$ in series R-L-C ckt is called the resonant freq. f_r .

At resonance $X_L = X_C$

$$2\pi f_r L = \frac{1}{2\pi f_r C}$$

$$f_r^2 = \frac{1}{4\pi^2 LC}$$

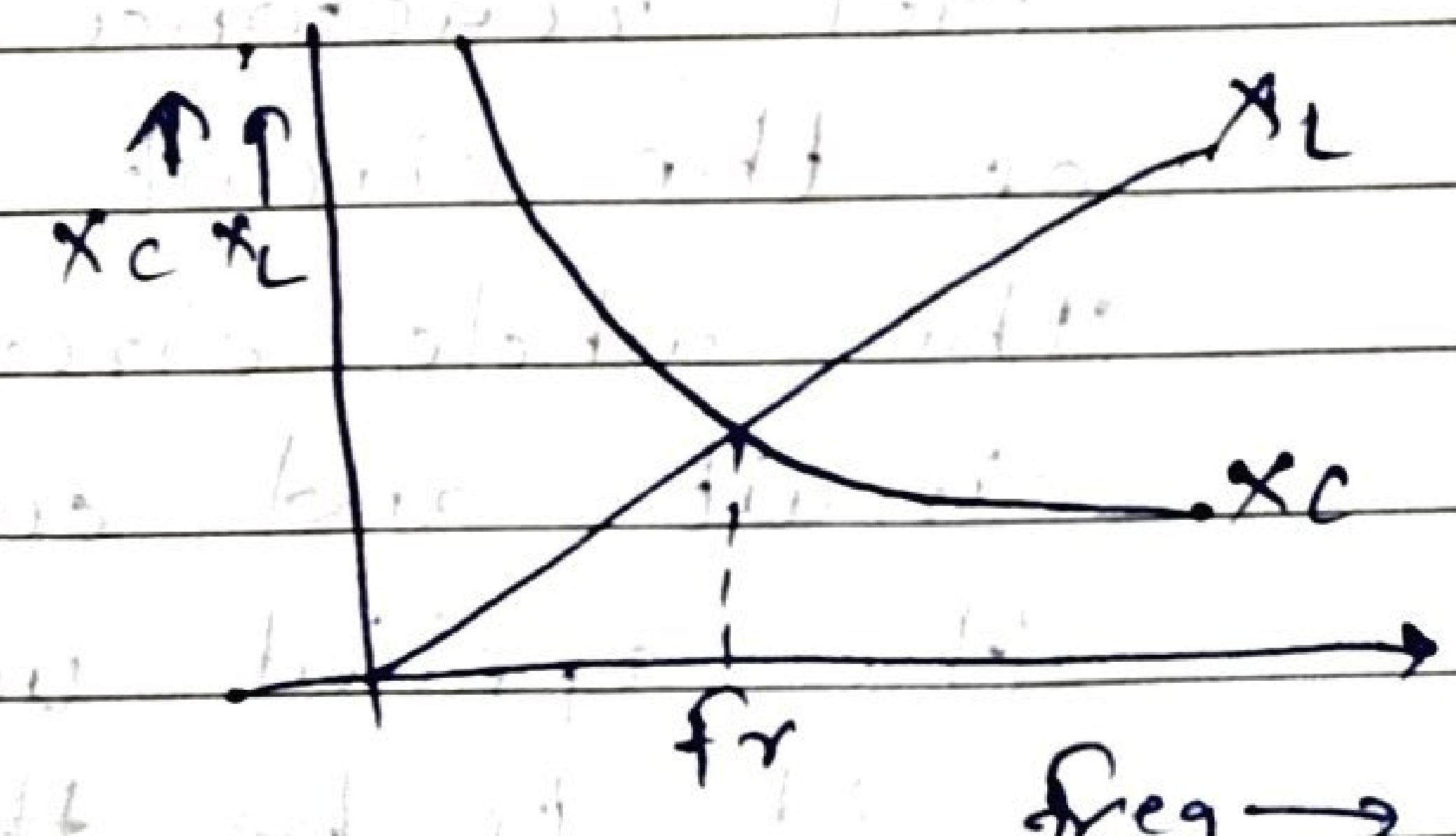


$$\therefore f_r = \frac{1}{2\pi\sqrt{LC}}, \text{ Hz}$$

Variation of reactances with freq.

$$\omega_r = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$

Resonance Curve :-

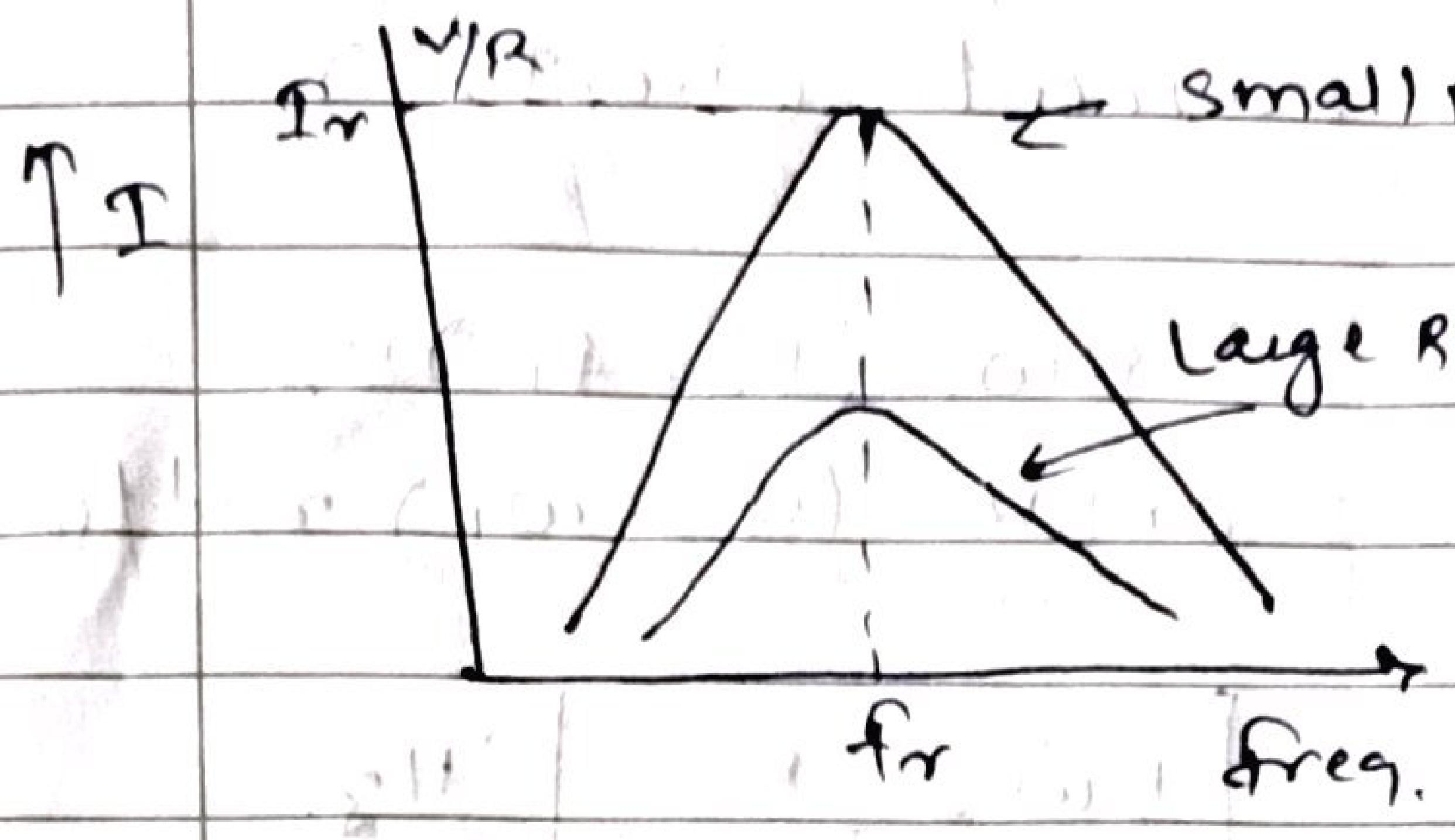The curve bet' current and freq. is known as resonance curve.



Below f_r

$X_C \rightarrow X_L$ & reactance is not zero.

Above f_r

$X_L \gg X_C$ & net reactance is not zero

So for both cases

circuit impedance will be greater than impedance $Z_r = R$ at resonance.

Shape of resonance curve depends upon value of resi.

Q-factor of series resonance ckt :-

$$Q\text{-factor} = \frac{\text{Voltage across } L \text{ or } C}{\text{Applied voltage}}$$

$$= \frac{V_L \text{ or } V_C}{V_R}$$

$$= \frac{V_L}{V_R} \quad (\text{AT resonance } V = V_R)$$

$$= \frac{I_r X_L}{I_r R}$$

$$= \frac{X_L}{R}$$


$$= \frac{2\pi f_r L}{R}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$\therefore Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Bandwidth of series resonance circuit :-

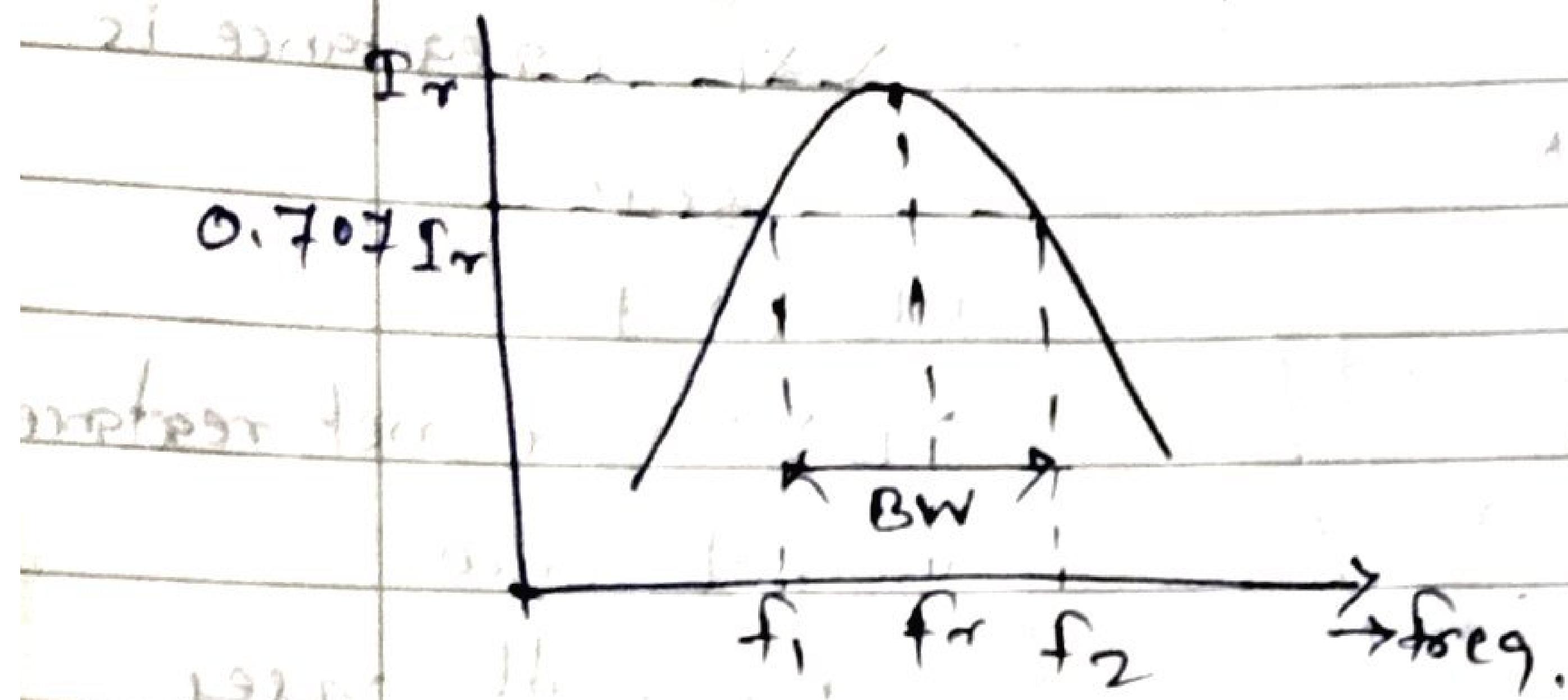Bandwidth :- The range of frequency over which circuit current is equal to or greater than 70.7% of max. current. (i.e. I_r)



$$BW = (f_2 - f_1) \text{ Hz}$$

$$\text{or } BW = (\omega_2 - \omega_1) \text{ rad/sec.}$$

$$BW = \frac{R}{2\pi L} \text{ Hz.}$$

f_1 - lower cut-off freq.

$$\text{or } BW = \frac{R}{L} \text{ rad/sec.}$$

f_2 - upper cut-off freq.

$$f_2 = f_r + \frac{BW}{2}$$

$$f_1 = f_r - \frac{BW}{2}$$

Relation betw Q factor & BW

$$Q \text{ factor} = \frac{2\pi f_r L}{R} \quad \left(\frac{2\pi L}{R} = \frac{1}{BW} \right)$$

$$\therefore Q \text{ factor} = \frac{f_r}{BW}$$

$$\text{or } f_r = Q \text{ factor} \times BW$$

Voltage drops at resonance:

$$V_R = I_r R = \frac{V}{R} \times R = V$$

$$V_L = I_r X_L$$

$$= \frac{V}{R} 2\pi f_r L \quad \left(f_r = \frac{1}{2\pi LC} \right)$$

$$\therefore V_L = \frac{V}{R} \frac{1}{2\pi LC} L$$

$$V_L = \frac{V}{R} \sqrt{\frac{L}{C}}$$

$$V_C = I_r X_C$$

$$= \frac{V}{R} \cdot \frac{1}{2\pi f_r C} \quad \left(f_r = \frac{1}{2\pi LC} \right)$$

$$= \frac{V}{R} \cdot \frac{1}{2\pi \cdot \frac{1}{2\pi LC} C}$$

$$\therefore V_C = \frac{V}{R} \sqrt{\frac{L}{C}}$$

Candidate Roll No. _____
(In figures)

Name: _____ Test Exam.

Date: _____ 20

Examination: _____ Branch/Semester _____

Subject: _____

Junior Supervisor's full
Signature with Date

Question No.	1	2	3	4	5	6	7	8	9	10	11	12	Total
Marks Obtained													


Admittance (\bar{Y})

$$\text{Admittance} = \bar{Y} = \frac{1}{\bar{Z}} = \frac{\bar{I}}{\bar{V}}$$

$$\text{or } \bar{Y} = \frac{1}{\bar{Z}} = \frac{\bar{I}}{\bar{V}}$$

Unit is mho (Ω)

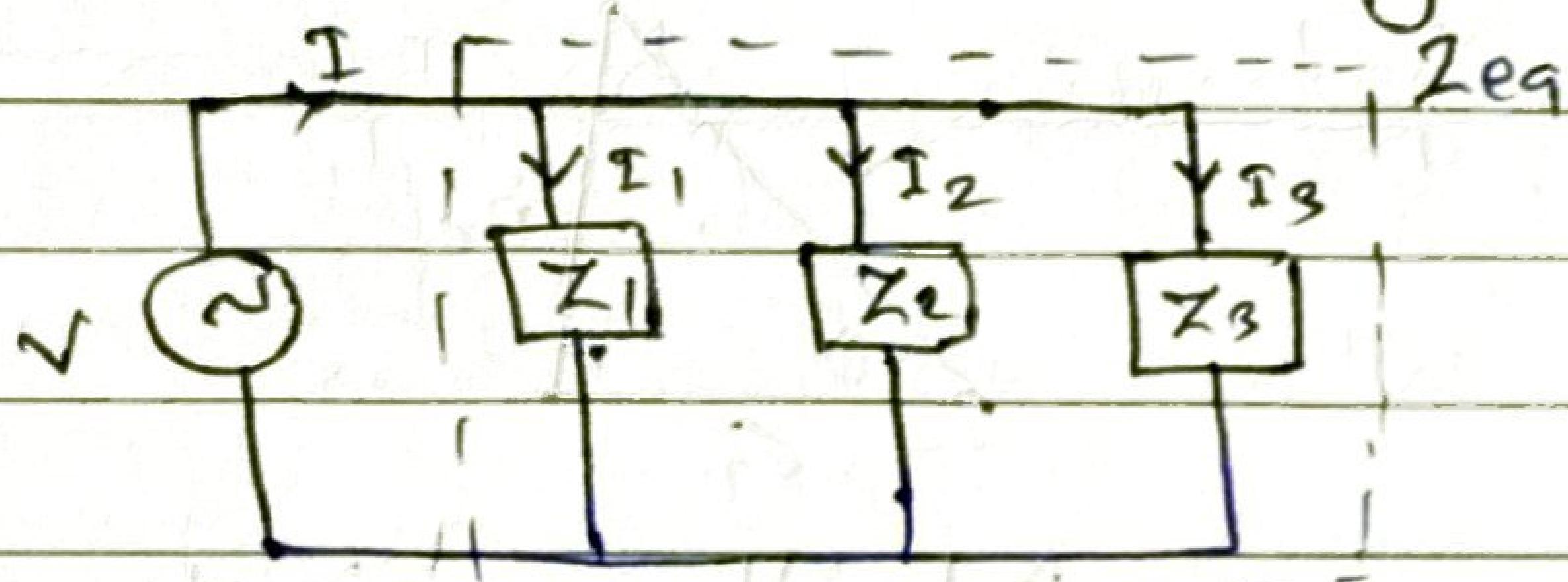- Circuit with higher value of admittance will have a higher value of current.



Parallel circuit

By law of parallel circuit

$$\frac{1}{\bar{Z}_{eq}} = \frac{1}{\bar{Z}_1} + \frac{1}{\bar{Z}_2} + \frac{1}{\bar{Z}_3}$$

$$\therefore \bar{Y}_{eq} = \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3$$

$$\text{Line current } \bar{I} = \frac{\bar{V}}{\bar{Z}_{eq}} = \bar{V} \bar{Y}_{eq}$$

In complex form admittance \bar{Y} can be expressed as

$$\bar{Y} = (G - jB_1)\bar{V} \quad \text{or} \quad \bar{Y} = (G + jB_c)\bar{V}$$

G = conductance ; in-phase component of \bar{Y}



B = Susceptance ; quadrature $\angle I - \angle V$

B_1 = inductive susceptance

B_c = capacitive

Admittance triangle :

① For inductive ckt

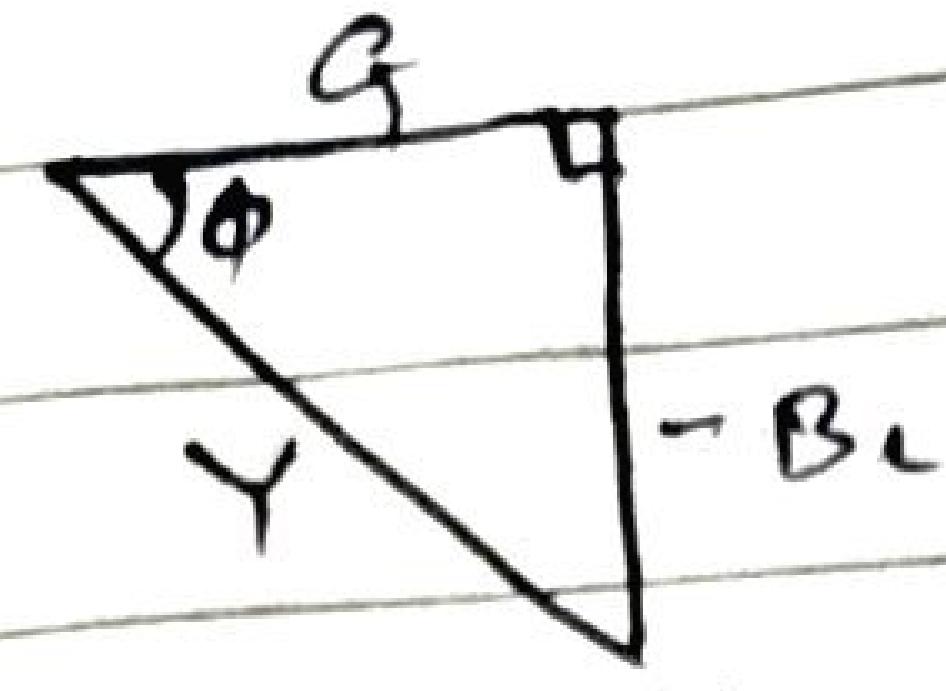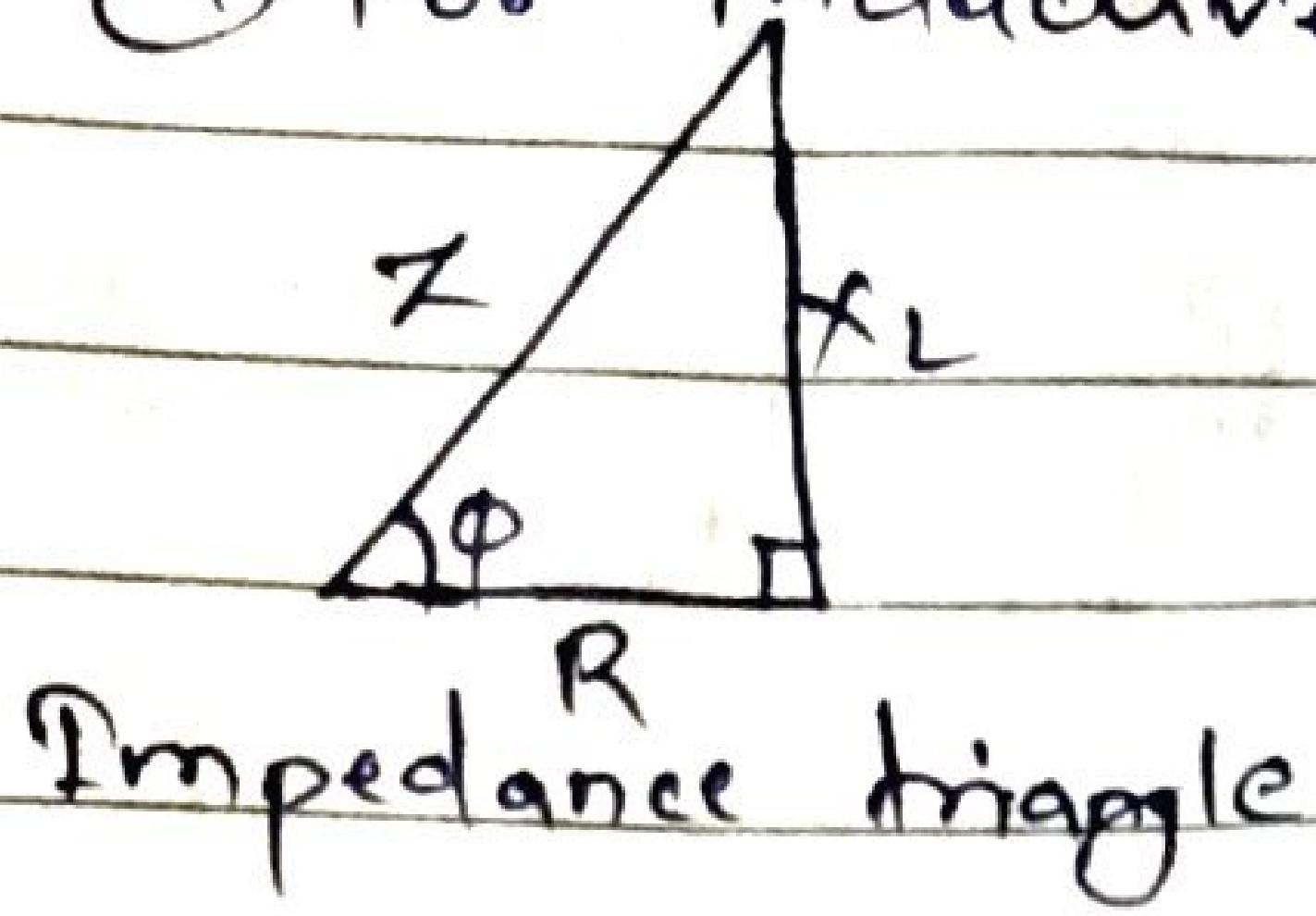

Admittance triangle



$$\text{Conductance } G = Y \cos \phi = \frac{1}{Z} \times \frac{R}{Z}$$

$$G = \frac{R}{Z^2} = \frac{R}{R^2 + X_L^2} \quad \text{v}$$

$$\text{Susceptance } B_L = Y \sin \phi = \frac{1}{Z} \times \frac{X_L}{Z}$$

$$B_L = \frac{X_L}{Z^2} = \frac{X_L}{R^2 + X_L^2} \quad \text{v}$$

② For capacitive circuit

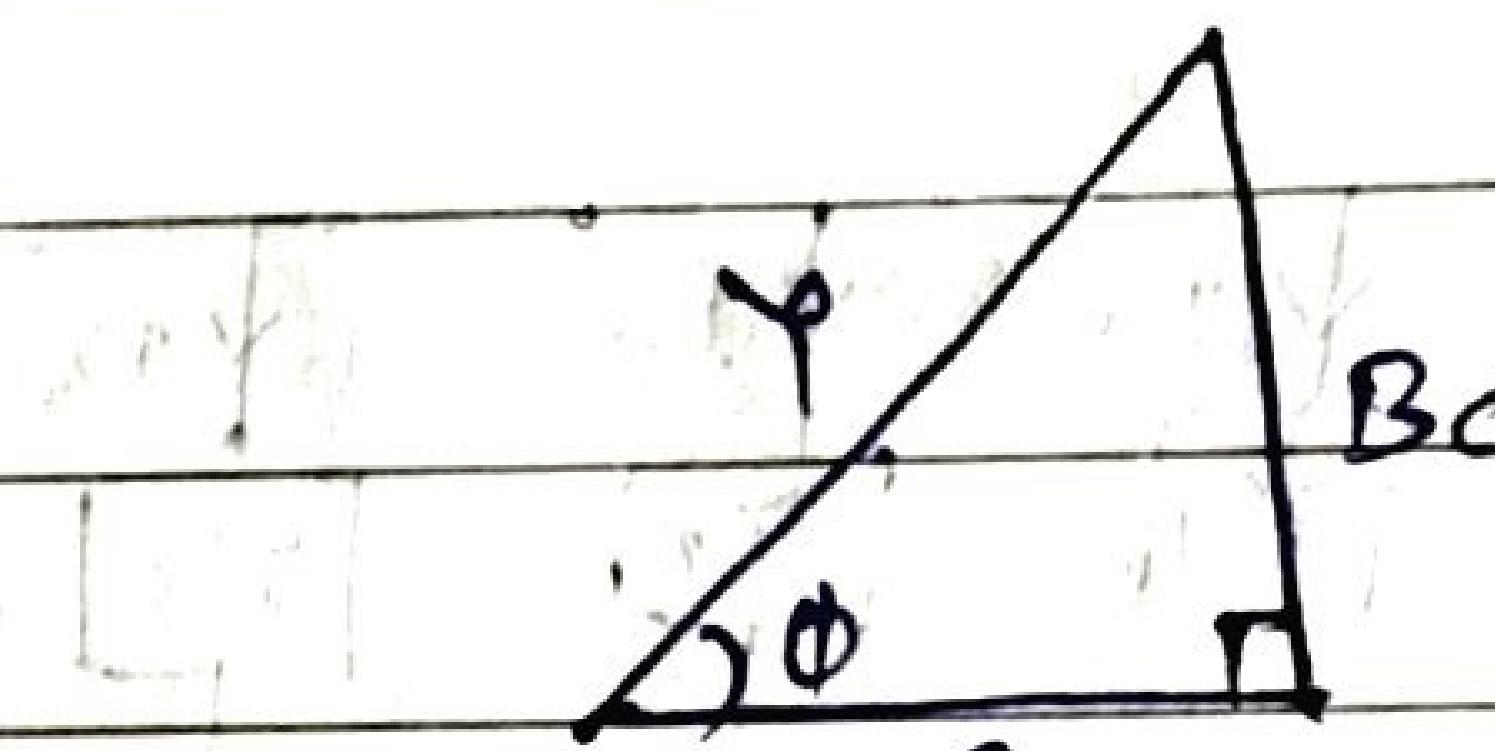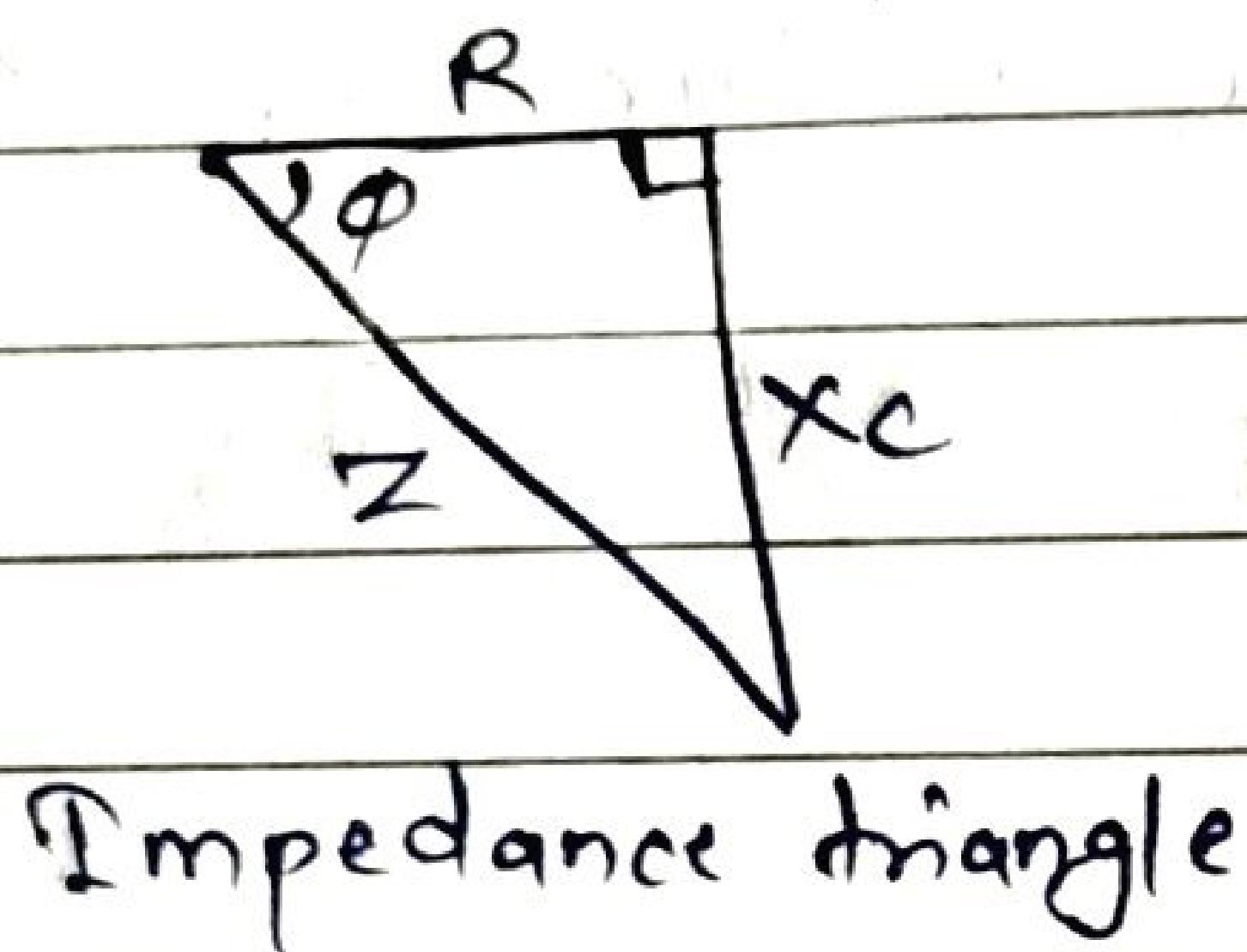

Admittance triangle


$$\text{Conductance } G = Y \cos \phi = \frac{1}{Z} \times \frac{R}{Z}$$

$$\therefore G = \frac{R}{Z^2} = \frac{R}{R^2 + X_C^2} \quad \text{v}$$

$$\text{Susceptance } B_C = Y \sin \phi = \frac{1}{Z} \times \frac{X_C}{Z}$$

$$\therefore B_C = \frac{X_C}{Z^2} = \frac{X_C}{R^2 + X_C^2} \quad \text{v}$$
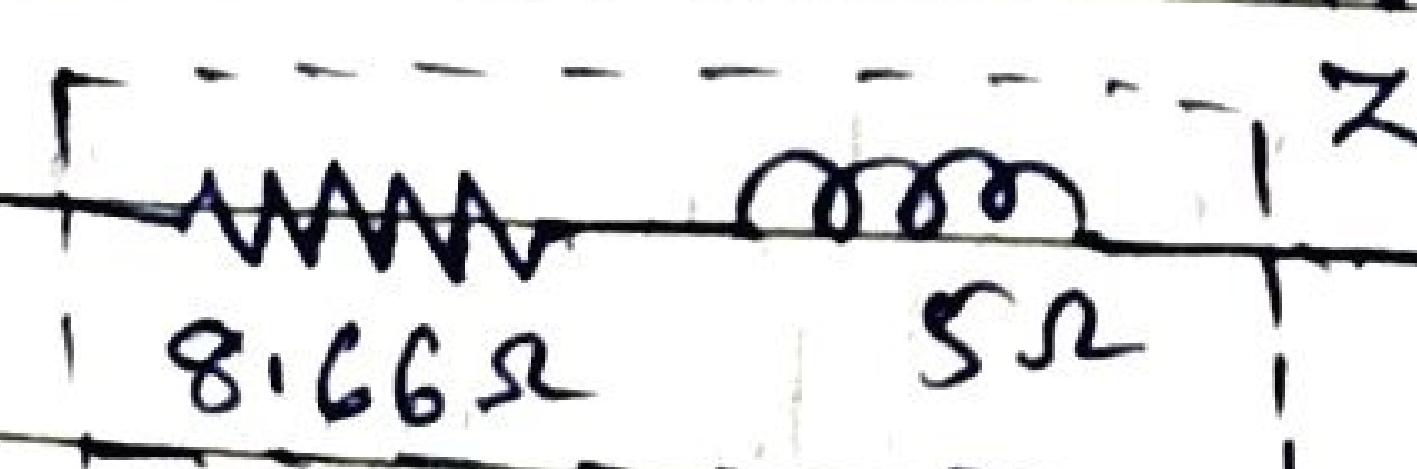
#1 Calculate the admittance \bar{Y} and draw the admittance triangle of following ckt.



$$\text{ckt impedance } \bar{Z} = (8.66 + j5) \Omega$$

$$= 10 / 30 \Omega$$

$$\text{ckt admittance } \bar{Y} = \frac{1}{\bar{Z}} = \frac{1}{10L30}$$


$$= (0.1L-30)\text{-}\omega$$

$$= (0.0866 - j0.05)\text{-}\omega$$

$$G = 0.0866\text{-}\omega$$

$$B_L = 0.05\text{-}\omega$$


Admittance triangle

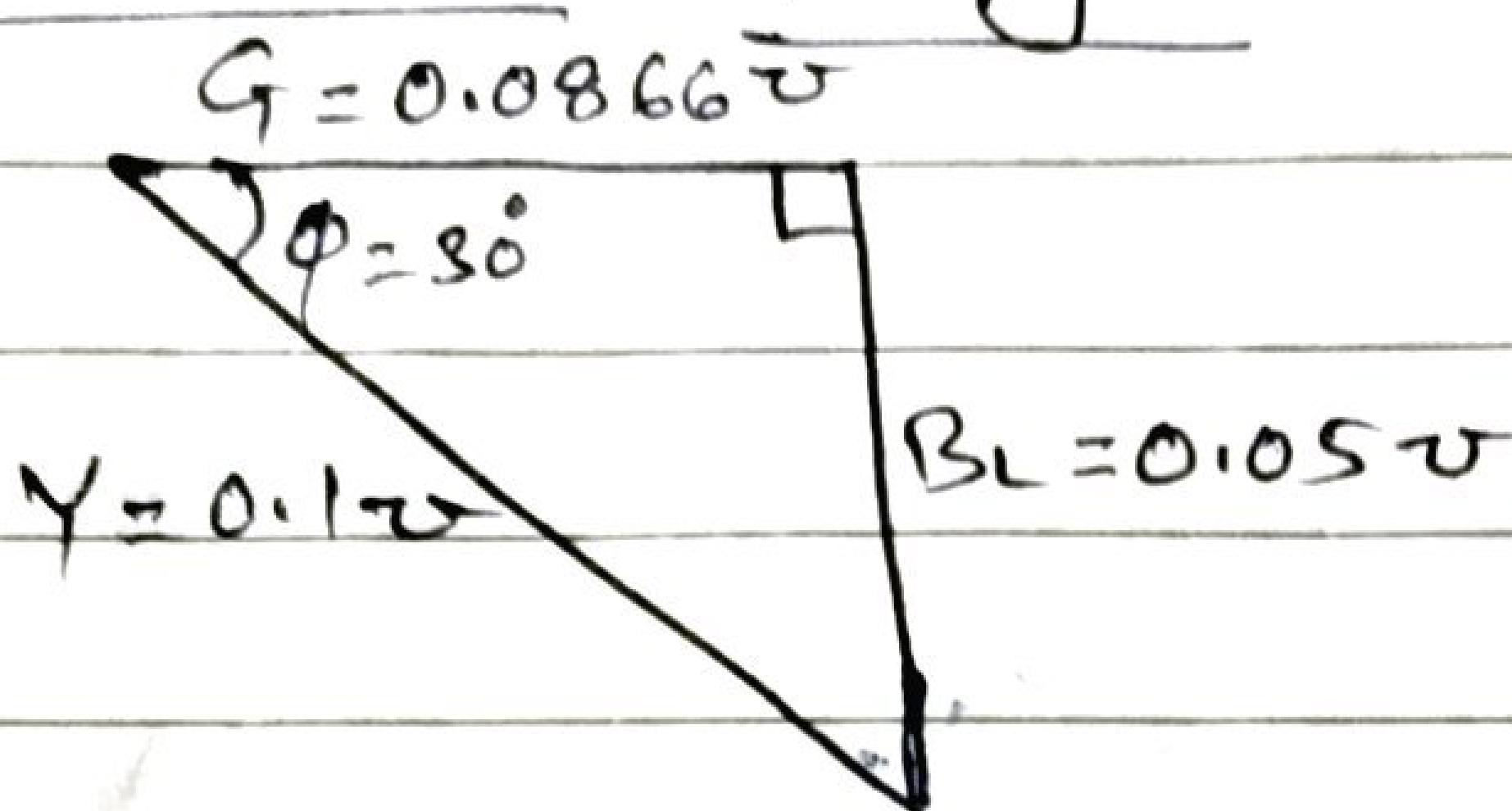
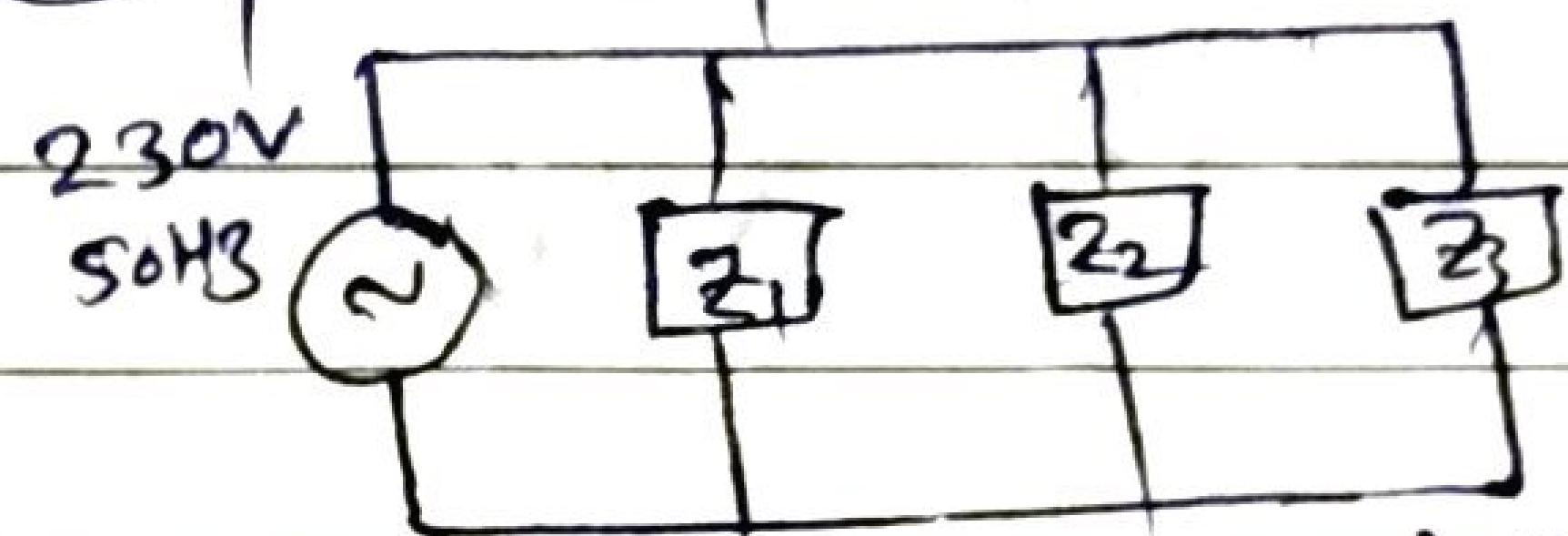
#2 For foll. ckt, determine ① admittance ② equivalent impedance ③ power consumed ④ power factor

Solution:-

$$\bar{Y} = \frac{1}{\bar{Z}_1} = \frac{1}{(10L30)} = (0.1L30)\text{-}\omega$$



$$\bar{Y}_2 = \frac{1}{\bar{Z}_2} = \frac{1}{(20L60)} = (0.05L-60)\text{-}\omega$$

$$Z_1 = (10L30)\text{-}\omega$$

$$Z_2 = (20L60)\text{-}\omega$$

$$Z_3 = (40L0)\text{-}\omega$$

$$\bar{Y}_3 = \frac{1}{\bar{Z}_3} = \frac{1}{(40L0)} = (0.025L0)\text{-}\omega$$

Total admittance of the ckt

$$\begin{aligned} ① \quad \bar{Y} &= \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 \\ &= (0.1L30) + (0.05L-60) + (0.025L0) \\ &= (0.0866 + j0.05) + (0.025 - j0.0433) + (0.025 + j0) \\ &= (0.1366 + j0.0067)\text{-}\omega \\ &= (0.137L2.81)\text{-}\omega \end{aligned}$$

② Equivalent impedance of the ckt

$$\bar{Z} = \frac{1}{\bar{Y}} = \frac{1}{(0.137L2.81)} = (7.3L-2.81)\text{-}\omega$$

$$③ \quad \text{Total current} = I = \frac{V}{\bar{Z}} = \frac{230}{7.3} = 31.51 \text{ Amp}$$

$$\begin{aligned} ④ \quad \text{Power factor} = \text{pf} &= \cos \phi = \cos (-2.81) \\ &= 0.998 \text{ leading} \end{aligned}$$