

Course Name:	Digital Design Laboratory	Semester:	III
Date of Performance:	02 / 08 / 2024	Batch No:	A1
Faculty Name:		Roll No:	16010123012
Faculty Sign & Date:		Grade/Marks:	___/25

Experiment No: 2
Title: Binary Adders and Subtractors

Aim and Objective of the Experiment:
To implement half and full adder-subtractor using gates and IC 7483

COs to be achieved:
CO2: Use different minimization technique and solve combinational circuits.

Tools used:
Trainer kits

Theory:
<p>Adder: The addition of two binary digits is the most basic operation performed by the digital computer. There are two types of adder:</p> <ul style="list-style-type: none"> • Half adder • Full adder <p>Half Adder: Half adder is a combinational logic circuit with two inputs and two outputs. It is the basic building block for the addition of two single-bit numbers.</p> <p>Full adder: A half adder has a provision not to add a carry coming from the lower order bits when multi-bit addition is performed. for this purpose, a third input terminal is added and this circuit is to add A, B, and C where A and B are the nth order bits of the number A and B respectively and C is the carry generated from the addition of (n-1) order bits. This circuit is referred to as full adder.</p> <p>Subtractor: Subtraction of two binary digits is one of the most basic operations performed by digital computer .there are two types of subtractors:</p> <ul style="list-style-type: none"> • Half subtractor • Full subtractor

Half subtractor: Logic circuit for the subtraction of B from A where A,B are 1 bit numbers is referred to as half subtract or .the subtract or process has two input and difference and borrow are the two outputs.

Full subtractor: As in the case of the addition using logic gates, a full subtractor is made by combining two half-sub tractors and an additional OR-gate. A full subtractor has the borrow in capability (denoted as BOR_{IN}) and so allows cascading which results in the possibility of multi-bit subtraction.

IC 7483

For subtraction of one binary number from another, we do so by adding 2's complement of the former to the latter number using a full adder circuit.

IC 7483 is a 16 pin, 4-bit full adder. This IC has a provision to add the carry output to transfer and end around carry output using Co and C4 respectively.

2's complement: 2's complement of any binary no. can be obtained by adding 1 in 1'scomplement of that no.


e.g. 2's complement of $+(10)_{10} = 1010$ is

$$\begin{array}{r} \text{1C of } 1010 \qquad 0101 \\ + \qquad \qquad \qquad 1 \\ \hline -(10)_{10} \qquad \qquad 0110 \end{array}$$


In 2's complement subtraction using IC 7483, we are representing negative number in 2's complement form and then adding it with 1st number.

Implementation Details:

Half Adder Block Diagram

 

Half Adder Circuit

 


Truth Table for Half Adder

Inputs		Outputs	
A	B	A	B
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


From the truth table (with steps):

A	B	Sum (S)	Carry (C)	Steps for Calculation
0	0	0	0	0 + 0 = 0, Sum = 0, Carry = 0
0	1	1	0	0 + 1 = 1, Sum = 1, Carry = 0
1	0	1	0	1 + 0 = 1, Sum = 1, Carry = 0
1	1	0	1	1 + 1 = 2, Sum = 0, Carry = 1

Full Adder Block Diagram

 

Full Adder Circuit

 


Truth Table for Full Adder

Inputs			Outputs	
A	B	C _{in}	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


From the truth table (with steps):

A	B	C_{in}	Sum (S)	Carry-out (C_{out})	Steps for Calculation
0	0	0	0	0	$0 + 0 + 0 = 0$, Sum = 0, Carry-out = 0
0	0	1	1	0	$0 + 0 + 1 = 1$, Sum = 1, Carry-out = 0
0	1	0	1	0	$0 + 1 + 0 = 1$, Sum = 1, Carry-out = 0
0	1	1	0	1	$0 + 1 + 1 = 2$, Sum = 0, Carry-out = 1
1	0	0	1	0	$1 + 0 + 0 = 1$, Sum = 1, Carry-out = 0
1	0	1	0	1	$1 + 0 + 1 = 2$, Sum = 0, Carry-out = 1
1	1	0	0	1	$1 + 1 + 0 = 2$, Sum = 0, Carry-out = 1
1	1	1	1	1	$1 + 1 + 1 = 3$, Sum = 1, Carry-out = 1

Half Subtractor Block Diagram

 

Half Subtractor Circuit

 

Half-Subtractor Circuit

Truth Table for Half Subtractor


A	B	Difference(D)	Borrow
0	0	0	0
0	1	1	1

1	0	1	0
1	1	0	0


From the truth table (with steps) :

A	B	Difference (D)	Borrow (B_{out})	Steps for Calculation
0	0	0	0	$0 - 0 = 0$, Difference = 0, Borrow = 0
0	1	1	1	$0 - 1 = -1$ (borrow 1), Difference = 1, Borrow = 1
1	0	1	0	$1 - 0 = 1$, Difference = 1, Borrow = 0
1	1	0	0	$1 - 1 = 0$, Difference = 0, Borrow = 0

Full Subtractor Block Diagram

 

Full Subtractor Circuit

 

Truth Table for Full subtractor

A	B	B _{IN}	D	BOR _{OUT}
---	---	-----------------	---	--------------------

0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

From the truth table (with steps):

A	B	B_{in}	Difference (D)	Borrow (B_{out})	Steps for Calculation
0	0	0	0	0	$0 - 0 - 0 = 0$, Difference = 0, Borrow = 0
0	0	1	1	1	$0 - 0 - 1 = -1$ (borrow 1), Difference = 1, Borrow = 1
0	1	0	1	1	$0 - 1 - 0 = -1$ (borrow 1), Difference = 1, Borrow = 1
0	1	1	0	1	$0 - 1 - 1 = -2$ (borrow 1), Difference = 0, Borrow = 1
1	0	0	1	0	$1 - 0 - 0 = 1$, Difference = 1, Borrow = 0
1	0	1	0	0	$1 - 0 - 1 = 0$, Difference = 0, Borrow = 0
1	1	0	0	0	$1 - 1 - 0 = 0$, Difference = 0, Borrow = 0
1	1	1	1	1	$1 - 1 - 1 = -1$ (borrow 1), Difference = 1, Borrow = 1

Example:

1) $7_{10} - 2_{10} = 5_{10}$

7 0111

2 0010

1'C of 2

1101


+ 1

2'C of 2


1110

$$0111 + \begin{array}{r} 1110 \\ 1 \\ \hline 0101 \end{array}$$


Pin Diagram IC7483

 

Adder

 

Subtractor

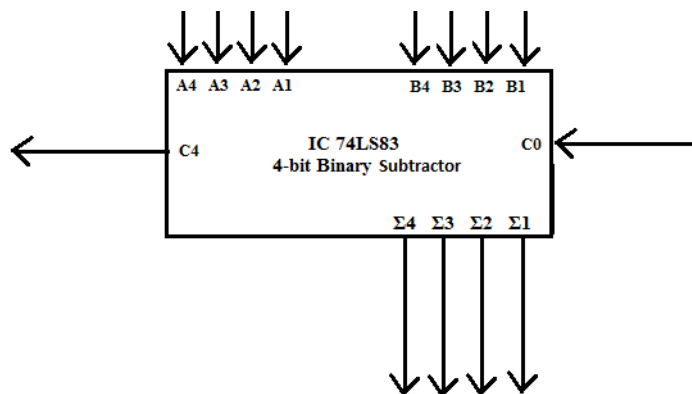

Implementation Details

Procedure:

- 1) Locate the IC 7483 and 4-not gates block on trainer kit.
- 2) Connect 1st input no. to A4-A1 input slot and 2nd (negative) no. to B4-B1 through 4-not gates (1C of 2nd no.)
- 3) Connect high input to Co so that it will get added with 1C of 2nd no. to get 2C.
- 4) Connect 4-bit output to the output indicators.
- 5) Switch ON the power supply and monitor the output for various input combinations.

Lab Work:

Exp2

Positive / Positive Combo -

+VE Add

9	00001001
+5	0000101
14	00001110

Positive / Negative Combo -

+ (-5)

9	00001001
+ (-5)	10111000
4	0100

8th bit = 0: Answer is +ve

Negative / Positive Combo -

+ (-9)

9	0111
+ (-5)	0101
-4	0100

8th bit = 1: Answer is -ve

Negative / Negative Combo -

2's complement of 2

(-2)	0010	1110
+ (-5)	1101	1011
-7	1110	1001

Sum

0010
1101
+ 1110
1110

0110
0111
0111 → 7

Adding two bits

Input		Output	
X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$C = XY$

$S = X'Y + XY'$
 $= X \oplus Y$

Adding three bits

Input			Output	
X	Y	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$S = \sum m(1, 2, 3, 4, 5, 6, 7)$

$= X'Y'C_{in} + X'YC_{in} + XY'C_{in} + XYC_{in}$

$= X'(Y'C_{in} + YC_{in}) + X(Y'C_{in} + YC_{in})$

$= X'(Y \oplus C_{in}) + X(Y \oplus C_{in})'$

$= X \oplus Y \oplus C_{in}$

$C_{out} = \sum m(3, 5, 6, 7)$


$= X'Y'C_{in} + X'YC_{in} + XY'C_{in} + XYC_{in}$

$= (X'Y + XY)C_{in} + XY(C_{in}' + C_{in})$

$= (X \odot Y)C_{in} + XY$


Full adder

For the 1st bit C_{in} is zero.

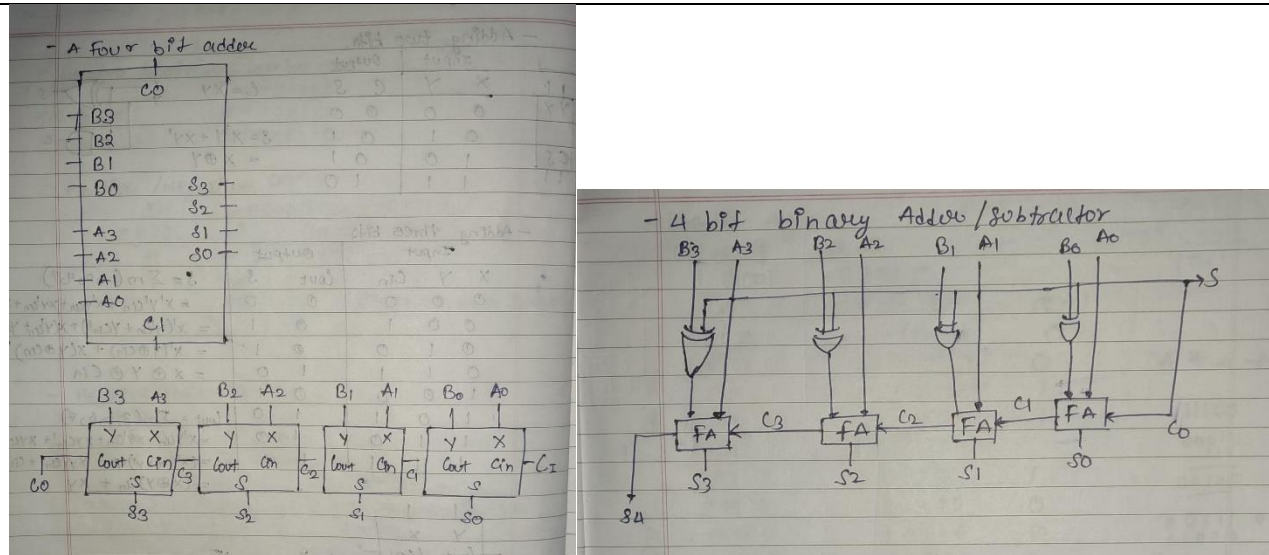

Post Lab Subjective/Objective type Questions:

 1. Design a full adder using two half adders.



2. Perform the following Binary subtraction with the help of appropriate ICs:
 - a. 6-4
 - b. 5-8
 - c. 7-9

Q2. a) $6 - 4 = 6 + (-4)$

$6 \Rightarrow 0110$, $4 \Rightarrow 0100$
 $-4 \Rightarrow 1100$

$\therefore \begin{array}{r} 0110 \\ + 1100 \\ \hline 0010 \end{array} \Rightarrow 2$

b) $5 - 8 = 5 + (-8)$

$5 \Rightarrow 00101$, $8 \Rightarrow 01000$, $-8 \Rightarrow 11000$

$\therefore \begin{array}{r} 00101 \\ + 11000 \\ \hline 11101 \end{array} \Rightarrow (-3)$

c) $7 - 9 = 7 + (-9)$

$7 \Rightarrow 00111$, $9 \Rightarrow 01001$, $-9 \Rightarrow 10111$

$\therefore \begin{array}{r} 00111 \\ + 10111 \\ \hline 10111 \end{array} \Rightarrow (-2)$

Conclusion:

We implemented half and full adder-subtractor circuits using the IC 7483, explored minimization techniques, and verified the circuits on the DDL kit.

Signature of faculty in-charge with Date: